



《芯片设计自动化与智能优化》 Boolean Algebra

The slides are based on Prof. Weikang Qian's lecture notes at SJTU and Prof. Rob Rutenbar's lecture notes at UIUC

Yibo Lin

Peking University

Outline


- Computational Boolean Algebra
 - Cofactors
 - Shannon expansion
 - Combinations of cofactors
 - Quantification
 - ~~— Tautology checking~~
 - ~~— Unateness~~
- Tautology and circuit representation
 - ~~— Recursive Tautology checking~~
 - Represent combinational circuits with DAG
 - Traversal combinational circuits: topological sorting
 - Circuit netlist format

Information Encoded to Boolean representation



图像编码

真彩色
(24位)

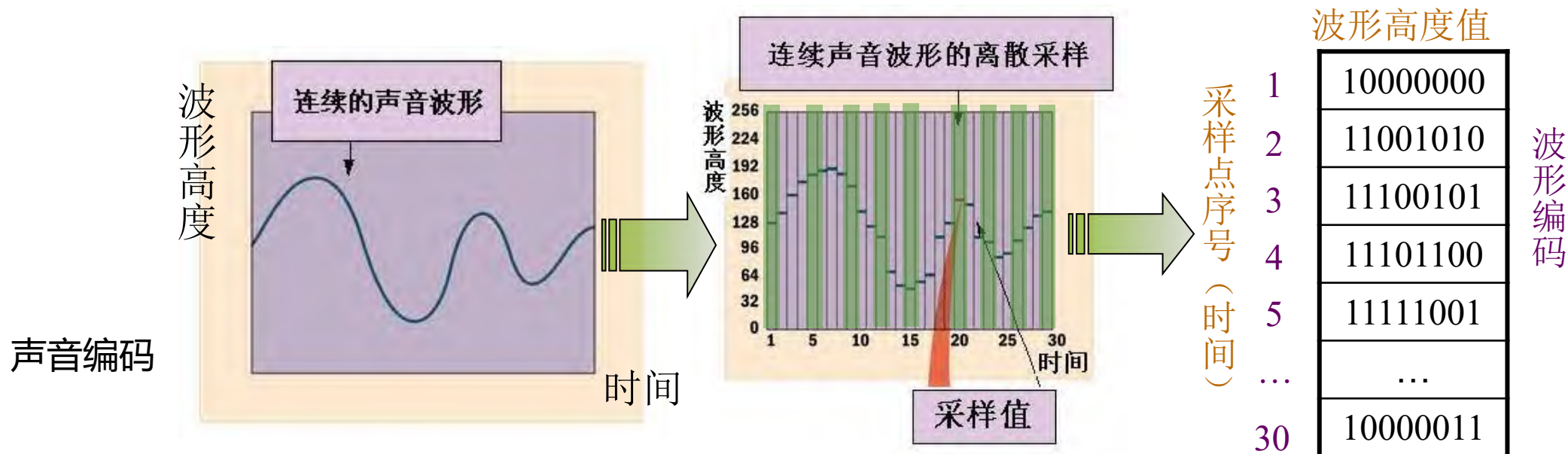

Boolean Algebra

➤ Karnaugh maps

- Given a truth table, simplify the Boolean expression

| A | B | C | Z |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$Z = f(A, B, C) = \overline{A}.\overline{B}.\overline{C} + \overline{A}.B + A.B.\overline{C} + A.C$$

| | | AB | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| C | 0 | 1 | 1 | 1 | |
| | 1 | | 1 | 1 | 1 |

$$\overline{A}.\overline{B}.\overline{C} + \overline{A}.B + A.B.\overline{C} + A.C$$

Boolean Algebra

- Karnaugh maps
 - Given a truth table, simplify the Boolean expression
 - **NOT sufficient** for real designs!
- Example: a multiplier of two 16-bit numbers
 - It has 32 inputs.
 - Its Karnaugh map has $2^{32} = 4,294,967,296$ squares
 - This is too big!
 - There must be a better way...

Computational Boolean Algebra

- Need **algorithmic**, **computational** strategies for Boolean stuff.
 - Need to be able to think of Boolean objects as **data structures + operators**
- What will we study?
 - **Decomposition strategies**
 - Ways of decomposing complex functions into simpler pieces.
 - A set of advanced concepts and terms you need to be able to do this.
 - **Computational strategies**
 - Ways to think about Boolean functions that let them be manipulated by programs.
 - **Interesting applications**
 - When you have new tools, there are some useful new things to do.

Advanced Boolean Algebra – Analogy to Calculus

- In calculus, you can represent complex functions like e^x using simpler functions.
 - If you can only use $1, x, x^2, x^3, \dots$ as the pieces ...
 - ... turns out $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$
- It corresponds to the **Taylor series expansion**.
 - $f(x) = f(0) + \frac{f'(0)}{1!} + \frac{f''(0)}{2!} + \frac{f'''(0)}{3!} + \dots$

Question: Anything like this for Boolean functions?

Yes. It is called **Shannon Expansion**.

Shannon Expansion

- Proposed by **Claude Shannon**, the father of information theory.
- Suppose we have a function $F(x_1, x_2, \dots, x_n)$.
- Define **a new function** if we set one of the $x_i = \text{const}$
 - $F(x_1, x_2, \dots, x_i = 1, \dots, x_n)$
 - $F(x_1, x_2, \dots, x_i = 0, \dots, x_n)$
- Example: $F(x, y, z) = xy + x\bar{z} + y(\bar{x}z + \bar{z})$
 - $F(x = 1, y, z) = y + \bar{z} + y\bar{z}$
 - $F(x, y = 0, z) = x\bar{z}$

Note: this is a new function, that no longer depends on the variable x_i .

Shannon Expansion: Cofactors

- Turns out to be an incredibly useful idea.
- It is also known as **Shannon cofactor** with respect to x_i .
 - We write $F(x_1, x_2, \dots, x_i = 1, \dots, x_n)$ as F_{x_i} . We call it **positive cofactor**.
 - We write $F(x_1, x_2, \dots, x_i = 0, \dots, x_n)$ as $F_{\bar{x}_i}$. We call it **negative cofactor**.
 - Often, just write them as $F(x_i = 1)$ and $F(x_i = 0)$.
- Why are these useful functions to get from F ?


Shannon Expansion Theorem

- Why we care: **Shannon Expansion Theorem**
- Given any Boolean function $F(x_1, x_2, \dots, x_n)$ and pick any x_i in F 's inputs, F can be represented as

$$F(x_1, x_2, \dots, x_n) = x_i \cdot F(x_i = 1) + \bar{x}_i \cdot F(x_i = 0)$$

- Proof:
 - Consider any $(x_1, x_2, \dots, x_n) \in \{0,1\}^n$
 - If $x_i = 1$:
 - If $x_i = 0$:

Shannon Expansion: Another View

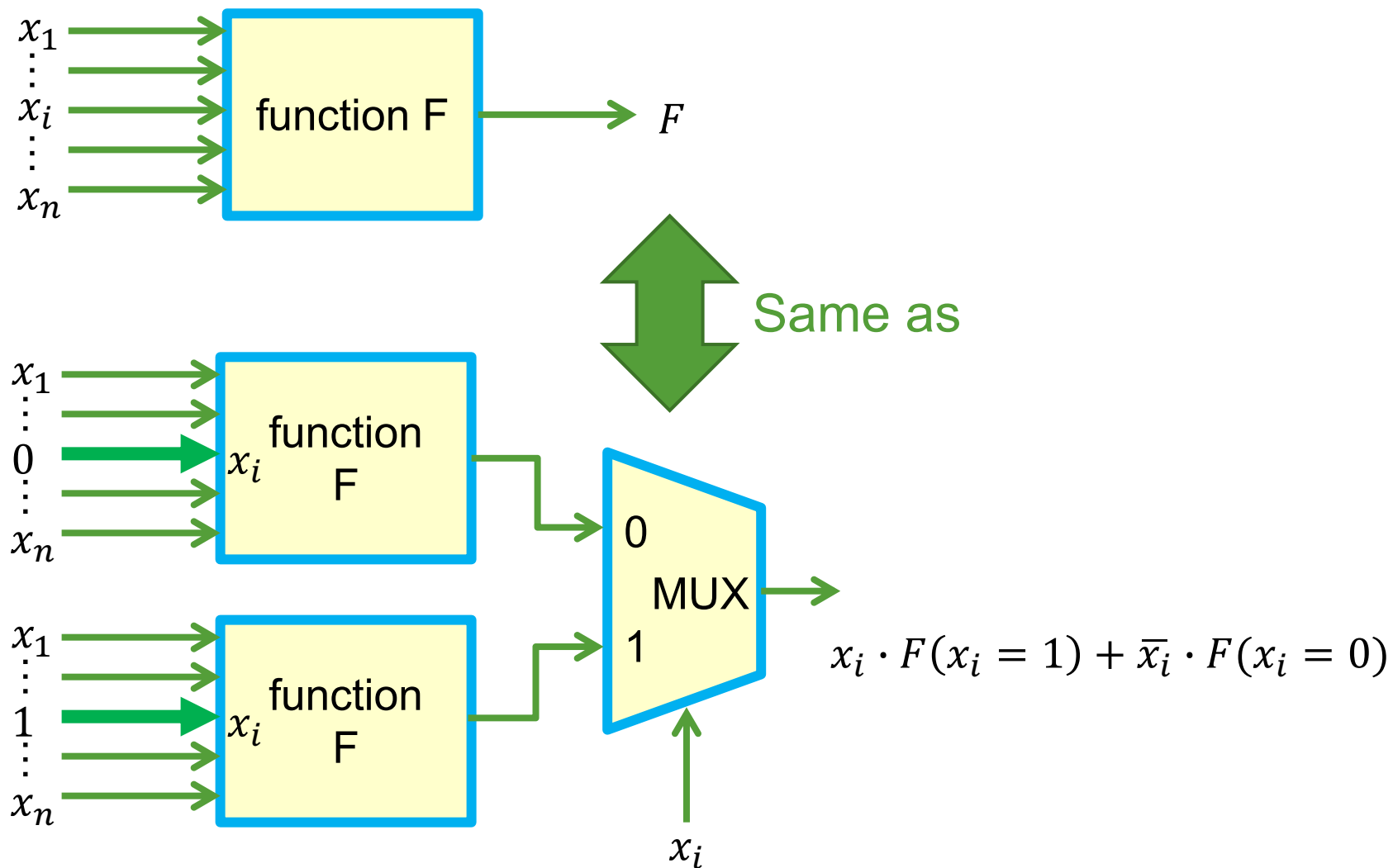

Shannon Expansion: Multiple Variables

- Can do it on **more than one** variable, too.
 - Just keep on applying the theorem on each variable.

- Example: Expand $F(x, y, z, w)$ around x and y

- First, expand around x :

$$F(x, y, z, w) = x \cdot F(x = 1) + \bar{x} \cdot F(x = 0)$$

- Then, expand cofactors $F(x = 1)$ and $F(x = 0)$ around y :

$$F(x = 1) = y \cdot F(x = 1, y = 1) + \bar{y} \cdot F(x = 1, y = 0)$$

$$F(x = 0) = y \cdot F(x = 0, y = 1) + \bar{y} \cdot F(x = 0, y = 0)$$

- Final result:

$$\begin{aligned} F(x, y, z, w) &= xy \cdot F(x = 1, y = 1) + x\bar{y} \cdot F(x = 1, y = 0) \\ &\quad + \bar{x}y \cdot F(x = 0, y = 1) + \bar{x}\bar{y} \cdot F(x = 0, y = 0) \end{aligned}$$

Shannon Cofactors: Multiple Variables

- There is notation for these multiple-variable expansions as well.
- Shannon cofactor with respect to x_i and x_j :
 - Write $F(x_1, \dots, x_i = 1, \dots, x_j = 0, \dots, x_n)$ as $F_{x_i \bar{x}_j}$.
 - The same for any number of variables x_i, x_j, x_k, \dots
 - Notice that order does **not** matter: $(F_x)_y = (F_y)_x = F_{xy}$.
- For the previous example:

$$F(x, y, z, w) = xy \cdot F_{xy} + x\bar{y} \cdot F_{x\bar{y}} + \bar{x}y \cdot F_{\bar{x}y} + \bar{x}\bar{y} \cdot F_{\bar{x}\bar{y}}$$
- Again, remember: each of the cofactors is a **function**, not a number.
 - $F_{xy} = F(x = 1, y = 1, z, w)$ is a Boolean **function** of z and w .

Properties of Cofactors

- What **else** can you do with cofactors?
- Suppose you have 2 functions $F(X)$ and $G(X)$, where $X = (x_1, x_2, \dots, x_n)$.
- Suppose you make a new function H , from F and G , say...
 - $H = \bar{F}$
 - $H = F \cdot G$, i.e., $H(X) = F(X) \cdot G(X)$
 - $H = F + G$, i.e., $H(X) = F(X) + G(X)$
 - $H = F \oplus G$, i.e., $H(X) = F(X) \oplus G(X)$
- Question: can you tell anything about H 's cofactors from those of F and G ?
 - $(F \cdot G)_x = \text{what?}$ $(\bar{F})_x = \text{what?}$

Nice Properties of Cofactors

- Cofactors of F and G tell you everything you need to know.
- Complements
 - $(\bar{F})_x = \overline{(F_x)}$
 - In English: cofactor of complement is complement of cofactor.
- Binary Boolean operators
 - $(F \cdot G)_x = F_x \cdot G_x$ cofactor of AND is AND of cofactors
 - $(F + G)_x = F_x + G_x$ cofactor of OR is OR of cofactors
 - $(F \oplus G)_x = F_x \oplus G_x$ cofactor of XOR is XOR of cofactors
- **Very useful!** Can often help in getting cofactors of complex formulas.


Combinations of Cofactors

- Now consider **operations** on cofactors themselves.
- Suppose we have $F(X)$, and get F_x and $F_{\bar{x}}$.
 - $F_x \oplus F_{\bar{x}} = ?$
 - $F_x \cdot F_{\bar{x}} = ?$
 - $F_x + F_{\bar{x}} = ?$
- Turns out these are all useful **new** functions.
 - Indeed, they even have **names**!
- Next: let's go look at these interesting, useful new functions.

Calculus Revisited: Derivatives

Remember how you defined derivatives?

- Suppose you have $y = f(x)$.

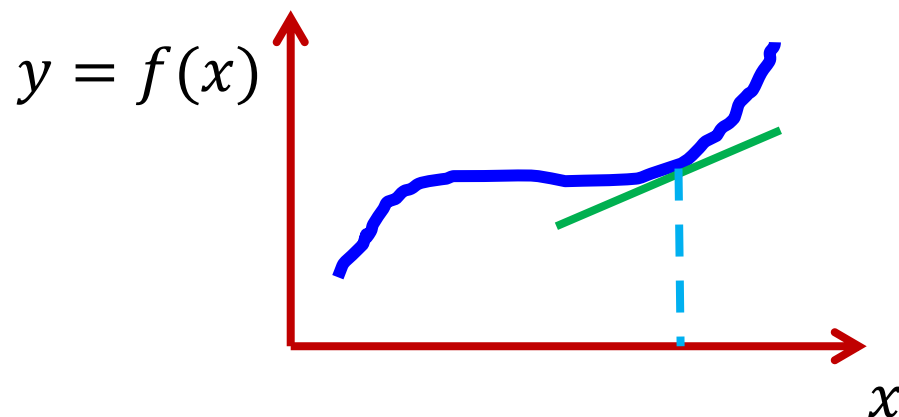

Defined as slope of curve as a function of point x .

How to compute?

$$\frac{df(x)}{dx} = \lim_{\Delta \rightarrow 0} \frac{f(x+\Delta) - f(x)}{\Delta}$$

Boolean Derivatives

► So, do Boolean functions have “**derivatives**”?

— Actually, yes. Trick is how to define them...

► Basic idea

- For real-valued $f(x)$, $\frac{df}{dx}$ tells how f changes when x changes.
- For 0,1-valued Boolean function, we cannot change x by small delta.
- Can only change $0 \leftrightarrow 1$, but can still ask how f changes with x ...
- For Boolean function $f(x)$, define

$$\frac{\partial f}{\partial x} = f_x \oplus f_{\bar{x}}$$

Boolean Derivatives

$$\frac{\partial f}{\partial x} = f_x \oplus f_{\bar{x}}$$

- Compare value of f when $x = 0$ against when $x = 1$.
- $\frac{\partial f}{\partial x} == 1$ if and only if $f(x = 0)$ is different from $f(x = 1)$.
- $\frac{\partial f}{\partial x}$ is also known as **Boolean difference**.

Boolean Difference

- Boolean difference also behaves sort of like regular derivatives...

- Order of variables does not matter

$$(\partial f / \partial x) / \partial y = (\partial f / \partial y) / \partial x$$

- Derivative of XOR is XOR of derivatives

$$\frac{\partial (f \oplus g)}{\partial x} = \frac{\partial f}{\partial x} \oplus \frac{\partial g}{\partial x}$$

— Like addition

- If function f is constant ($f = 1$ or $f = 0$ for all inputs), then $\partial f / \partial x = 0$ for any x .

Boolean Difference

- But some things are just more complex
 - Derivatives of $(f \cdot g)$ and $(f + g)$ do not work the same...

$$\frac{\partial}{\partial x}(f \cdot g) = \left[f \cdot \frac{\partial g}{\partial x} \right] \oplus \left[g \cdot \frac{\partial f}{\partial x} \right] \oplus \left[\frac{\partial f}{\partial x} \cdot \frac{\partial g}{\partial x} \right]$$

$$\frac{\partial}{\partial x}(f + g) = \left[\bar{f} \cdot \frac{\partial g}{\partial x} \right] \oplus \left[\bar{g} \cdot \frac{\partial f}{\partial x} \right] \oplus \left[\frac{\partial f}{\partial x} \cdot \frac{\partial g}{\partial x} \right]$$

- Why?

- Because AND and OR on Boolean values do not always behave like **ADDITION** and **MULTIPLICATION** on real numbers.

Boolean Difference: Gate-Level View

➤ Consider simple examples for $\partial f / \partial x$.

➤ Inverter: $f = \bar{x}$

– $f_x = 0, f_{\bar{x}} = 1, \partial f / \partial x = f_x \oplus f_{\bar{x}} = 1$

➤ AND: $f = xy$

– $f_x = y, f_{\bar{x}} = 0, \partial f / \partial x = f_x \oplus f_{\bar{x}} = y$

➤ OR: $f = x + y$


– $f_x = 1, f_{\bar{x}} = y, \partial f / \partial x = f_x \oplus f_{\bar{x}} = \bar{y}$

➤ XOR: $f = x \oplus y$

– $f_x = \bar{y}, f_{\bar{x}} = y, \partial f / \partial x = f_x \oplus f_{\bar{x}} = 1$

Meaning: When $\partial f / \partial x = 1$, then f changes if x changes!

Interpreting the Boolean Difference

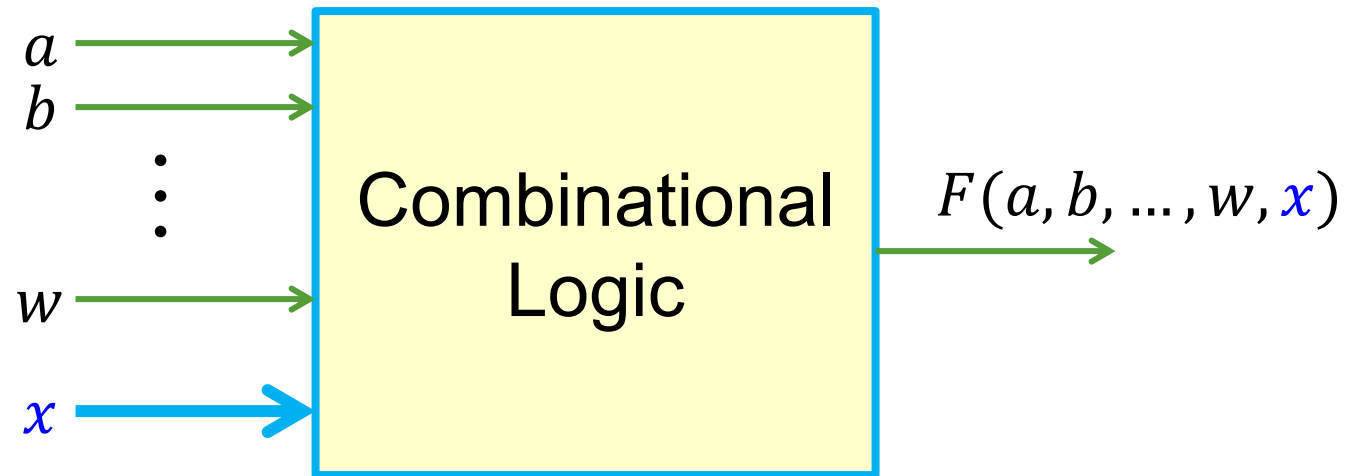

- What does $\partial F(a, b, \dots, w, x) / \partial x = 1$ mean?
 - If you apply a pattern of inputs (a, b, \dots, w) that makes $\partial F / \partial x = 1$, then any change in x will force a change in output F .

Boolean Difference: Example



$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = ab + ac_{in} + bc_{in}$$

► What is $\partial c_{out} / \partial c_{in} = 1$?

— $c_{out}(c_{in} = 1) = a + b$

— $c_{out}(c_{in} = 0) = ab$

— $\partial c_{out} / \partial c_{in} = c_{out}(c_{in} = 1) \oplus c_{out}(c_{in} = 0)$
 $= (a + b) \oplus (ab) = a \oplus b$

► Make sense?

— $a \oplus b = 1 \Rightarrow a \neq b$

Boolean Difference: Summary

- Boolean difference explains under what situations an input-change can cause output-change for a Boolean function f .
- $\partial f / \partial x$ is another Boolean function, but it does not depend on x !
 - It cannot, because it is made out of cofactors with respect to x , which eliminate all the x and \bar{x} terms by setting them to constants.
- **Very useful!** (we will see more, later...)


AND of F_x and $F_{\bar{x}}$: Universal Quantification

➤ AND the cofactors: $F_{x_i} \cdot F_{\bar{x}_i}$

- Name: **Universal Quantification** of function F with respect to variable x_i .
- Represented as: $(\forall x_i F)(x_1, x_2, \dots, x_{i-1}, x_{i+1}, \dots, x_n)$

➤ $(\forall x_i F)$ is a new function

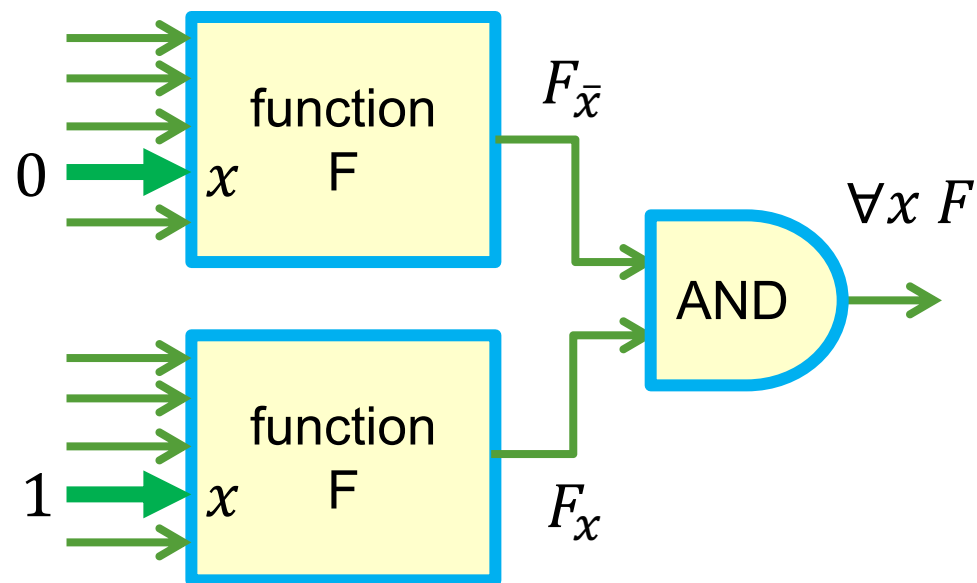- It does not depend on x_i !
- “ \forall ” sign is the “for all” symbol from logic.



OR of F_x and $F_{\bar{x}}$: Existential Quantification

► OR the cofactors: $F_{x_i} + F_{\bar{x}_i}$

– Name: **Existential Quantification** of function F with respect to variable x_i .


– Represented as: $(\exists x_i F)(x_1, x_2, \dots, x_{i-1}, x_{i+1}, \dots, x_n)$

► $(\exists x_i F)$ is a new function


– It does not depend on x_i !

– “ \exists ” sign is the “there exists” symbol from logic.

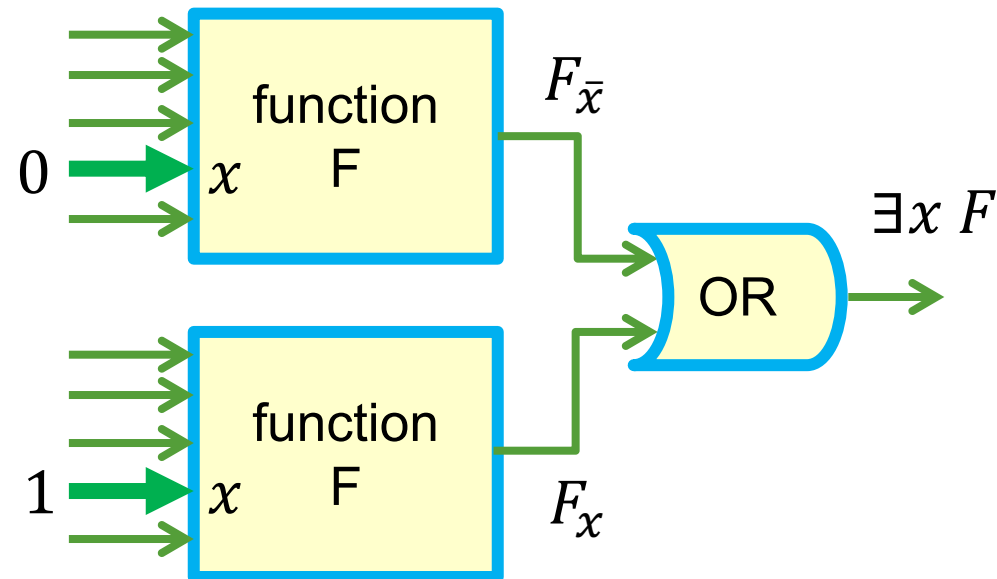Both $\forall x_i F$ and $\exists x_i F$ do not depend on x_i




Quantification Notation Makes Sense...

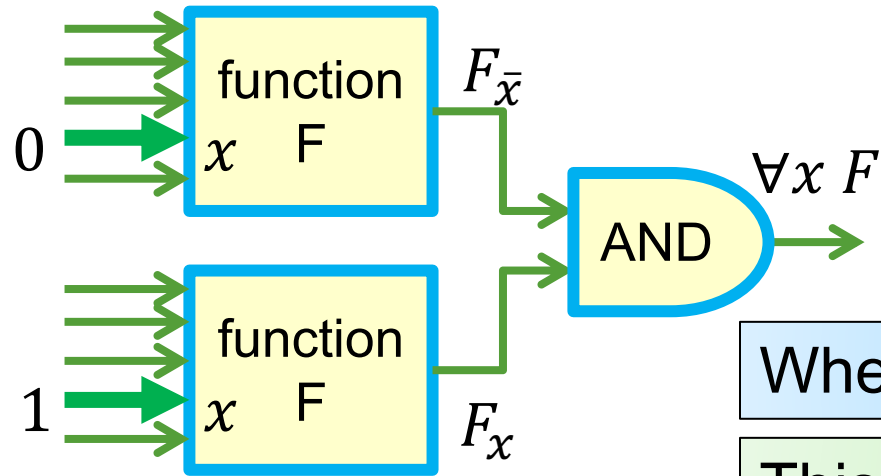

When does $\forall x F$ (all vars except x) = 1?

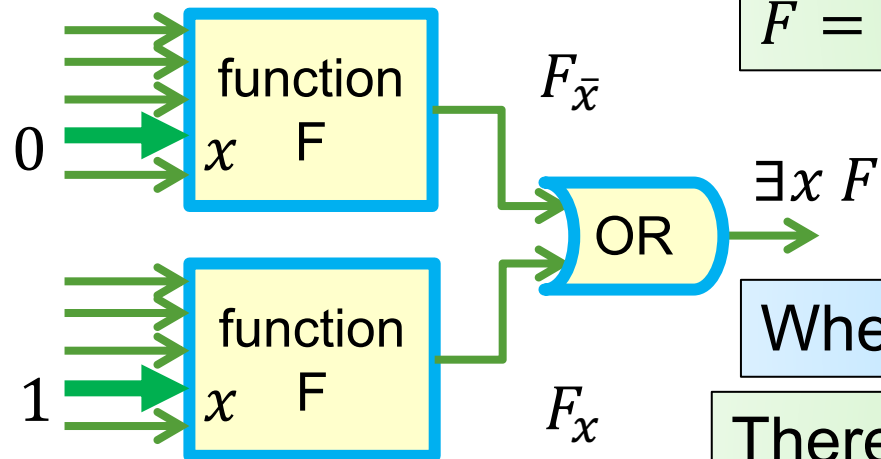This input pattern of **the other** vars makes $F = 1$ for all values of x .



When does $\exists x F$ (all vars except x) = 1?

There exists a value of x that makes $F = 1$ for this input pattern of **the other** vars.

Quantification: Gate-Level View

- Consider simple examples for $(\forall x f)$ and $(\exists x f)$.
- Inverter: $f = \bar{x}$
 - $f_x = 0, f_{\bar{x}} = 1, (\forall x f) = f_x f_{\bar{x}} = 0, (\exists x f) = f_x + f_{\bar{x}} = 1$
- AND: $f = xy$
 - $f_x = y, f_{\bar{x}} = 0, (\forall x f) = f_x f_{\bar{x}} = 0, (\exists x f) = f_x + f_{\bar{x}} = y$
- OR: $f = x + y$
 - $f_x = 1, f_{\bar{x}} = y, (\forall x f) = f_x f_{\bar{x}} = y, (\exists x f) = f_x + f_{\bar{x}} = 1$
- XOR: $f = x \oplus y$
 - $f_x = \bar{y}, f_{\bar{x}} = y, (\forall x f) = f_x f_{\bar{x}} = 0, (\exists x f) = f_x + f_{\bar{x}} = 1$

Make sense?

Extends to More Variables in Obvious Way

- ▶ Like Boolean difference, can do with respect to more than 1 variable

- Suppose we have $F(x, y, z, w)$.
- $(\forall xy F)(z, w) = (\forall x (\forall y F)) = F_{xy} \cdot F_{x\bar{y}} \cdot F_{\bar{x}y} \cdot F_{\bar{x}\bar{y}}$
- $(\exists xy F)(z, w) = (\exists x (\exists y F)) = F_{xy} + F_{x\bar{y}} + F_{\bar{x}y} + F_{\bar{x}\bar{y}}$

- ▶ Remember:


- $(\forall x F)$, $(\exists x F)$, and $\partial F / \partial x$ are all functions.
- ... but they are functions of all the variables **except** x .

Quantification Example


- Consider the following circuit, it adds $x = 0$ or $x = 1$ to a 2-bit number a_1a_0 .
 - It's just a 2-bit adder, but instead of b_1b_0 for the second operand, it is just $0x$.
 - It has a carry-in d and produces a carry-out c .
 - Hence, c is function of a_1, a_0, d and x .

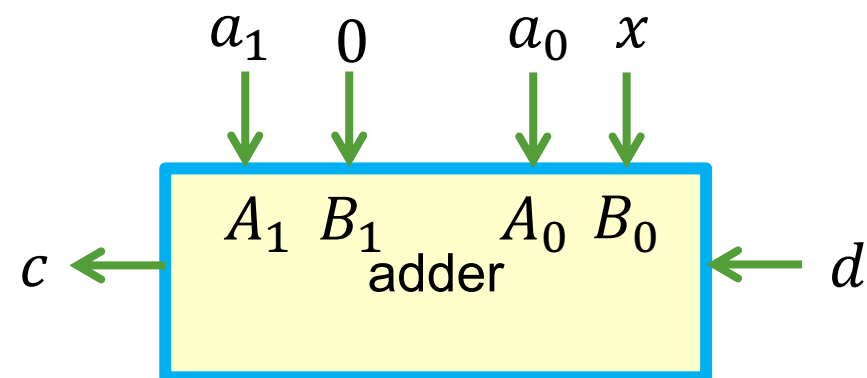- Questions:

- What is $(\forall a_1 a_0 c)(x, d)$?
- What is $(\exists a_1 a_0 c)(x, d)$?



Quantification Example

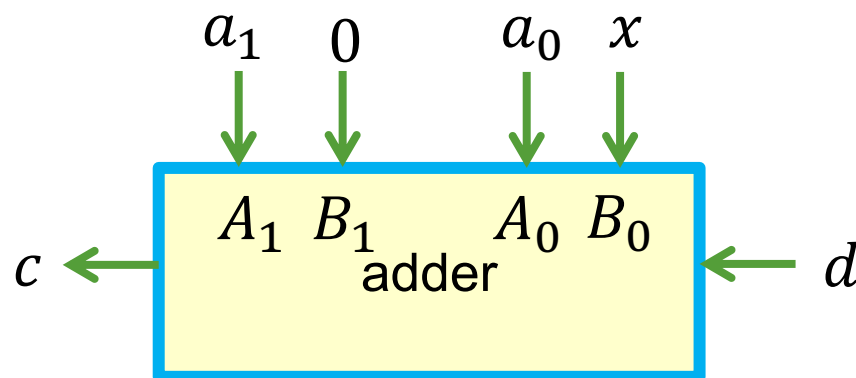


➤ What is $(\forall a_1 a_0 c)(x, d)$?

- A function of only x and d . Makes a 1 for values of x and d that make a carry $c = 1$ for **all values** of inputs a_1 and a_0 .

➤ What is $(\exists a_1 a_0 c)(x, d)$?

- A function of only x and d . Makes a 1 for values of x and d that make a carry $c = 1$ for **some value** of inputs a_1 and a_0 , i.e., there exists some a_1 and a_0 that for this x and d , $c = 1$.

Quantification Example

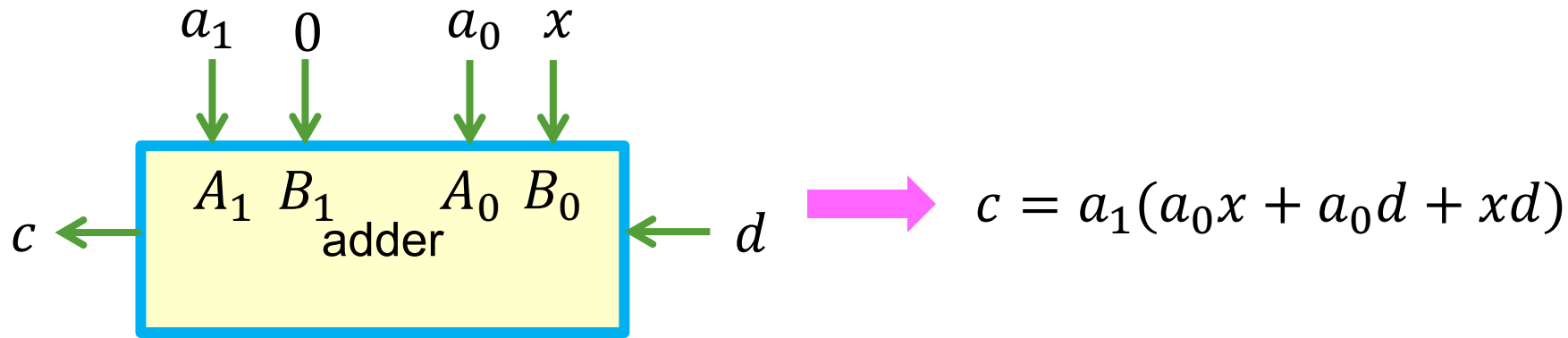

► Compute $(\forall a_1 a_0 c)(x, d)$

$$- c_{a_1 a_0} \cdot c_{a_1 \bar{a}_0} \cdot c_{\bar{a}_1 a_0} \cdot c_{\bar{a}_1 \bar{a}_0} \\ = 0$$


► Compute $(\exists a_1 a_0 c)(x, d)$

$$- c_{a_1 a_0} + c_{a_1 \bar{a}_0} + c_{\bar{a}_1 a_0} + c_{\bar{a}_1 \bar{a}_0} \\ = x + d$$

Need four cofactors:

- $c_{a_1 a_0} = x + d$
- $c_{a_1 \bar{a}_0} = xd$
- $c_{\bar{a}_1 a_0} = 0$
- $c_{\bar{a}_1 \bar{a}_0} = 0$

Quantification Example

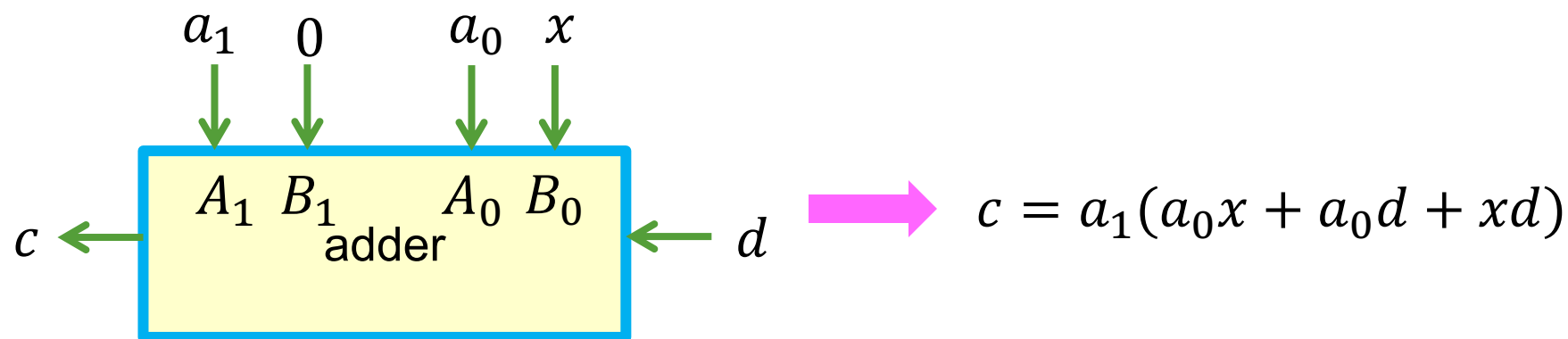

➤ $(\forall a_1 a_0 c)(x, d) = 0$


— Make sense: **No** values of x and d that make $c = 1$ **independent of** a_1 and a_0

➤ $(\exists a_1 a_0 c)(x, d) = x + d$

— Make sense: If **at least one** of x and $d = 1$, then **there exists** a_1 and a_0 that let $c = 1$.

Quantification Application: Network Repair


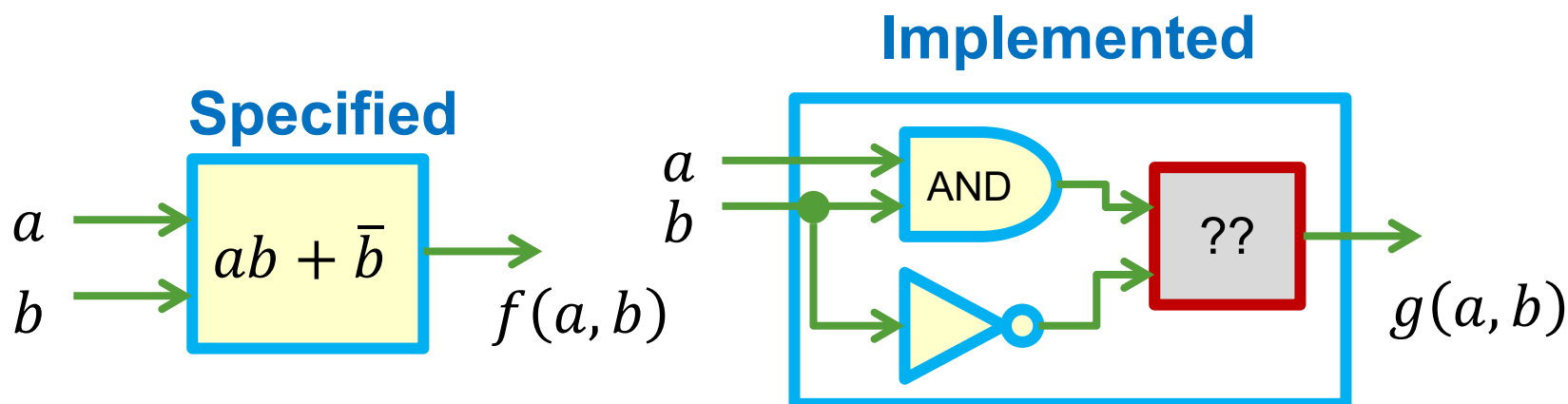
- Suppose that someone specified a logic block for you to implement: $f(a, b) = ab + \bar{b}$
 - ...but you implemented it **wrong**: in particular, you got ONE gate wrong.



- Goal
 - Can we deduce how precisely to **change this gate** to restore correct function?
 - Go with this very trivial test case to see how mechanics work...


Network Repair

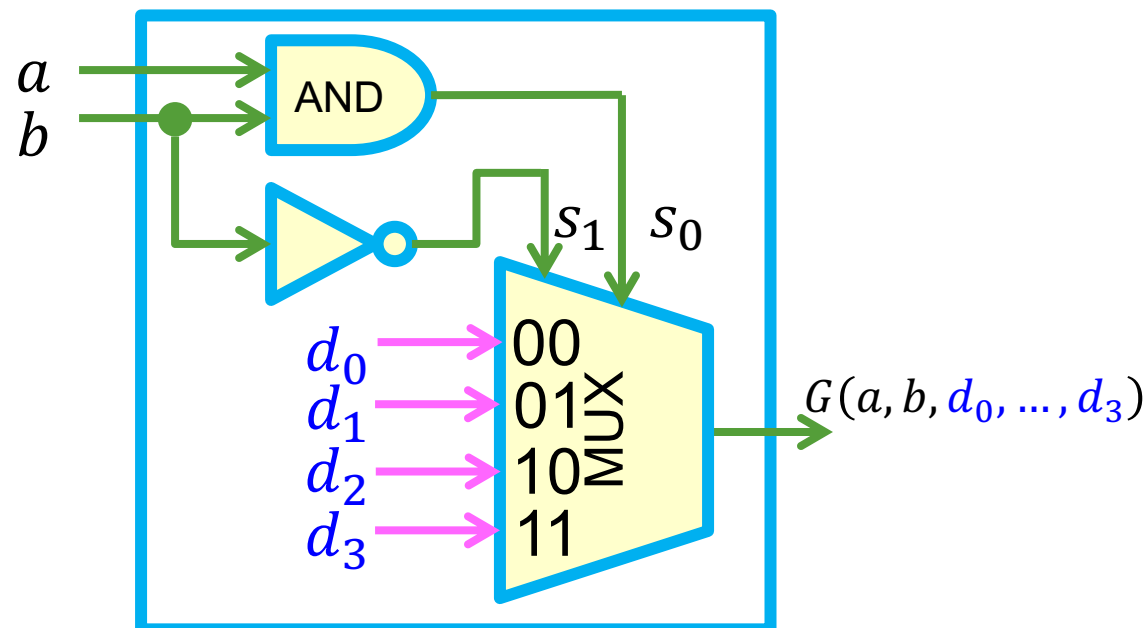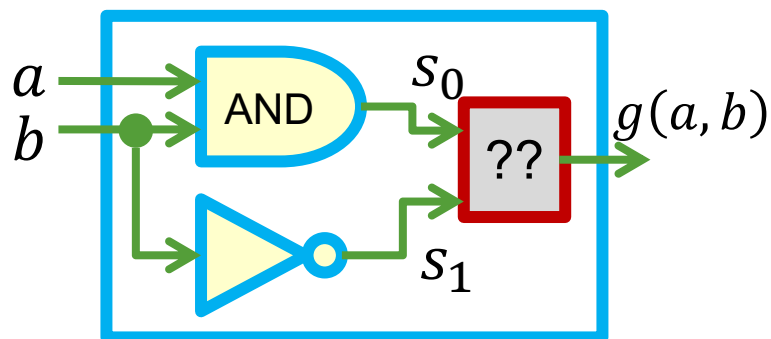- Clever trick: Replace our suspect gate by a 4-to-1 MUX with 4 arbitrary new vars d_0, d_1, d_2, d_3 .
 - By cleverly assigning values to d_0, d_1, d_2, d_3 , we can **fake** any gate.
 - Question is: what are the right values of d_i 's so g is repaired, i.e., $g = f$?




Aside: Faking a Gate with a MUX

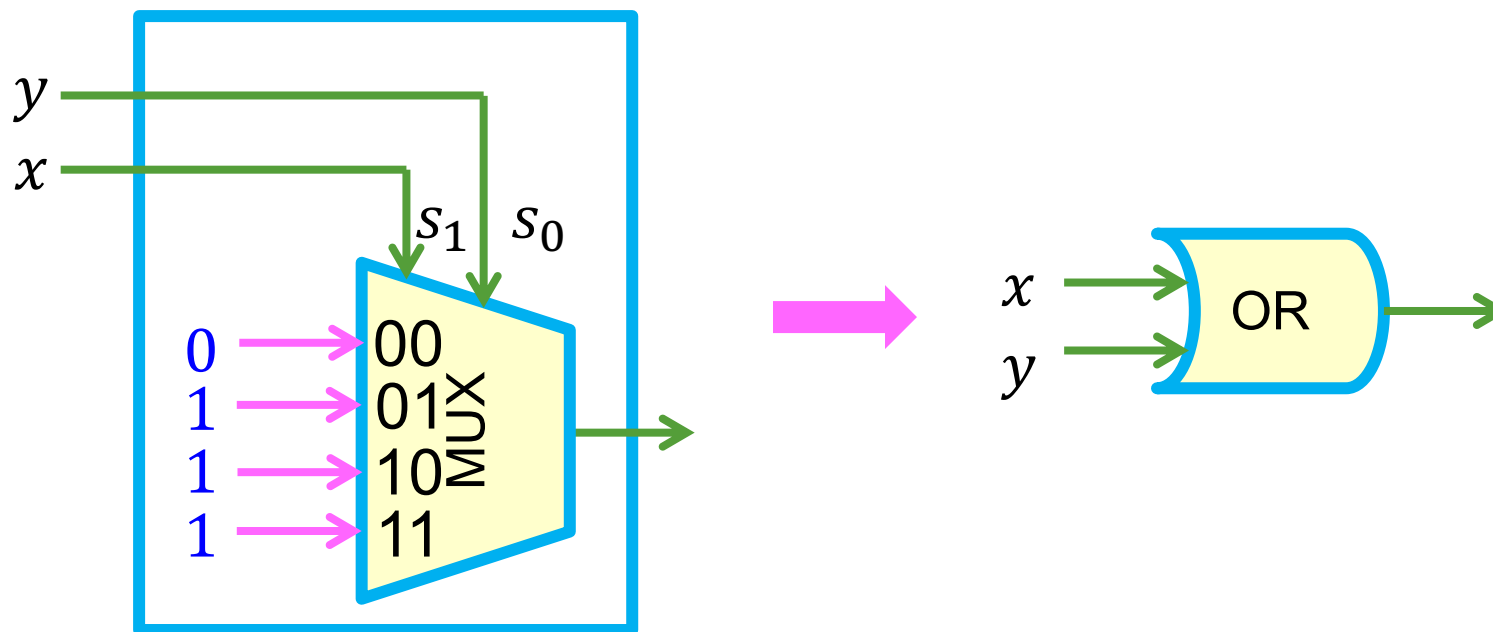- You can do **any** function of 2 vars with one 4-to-1 multiplexor (MUX).




Aside: Faking a Gate with a MUX

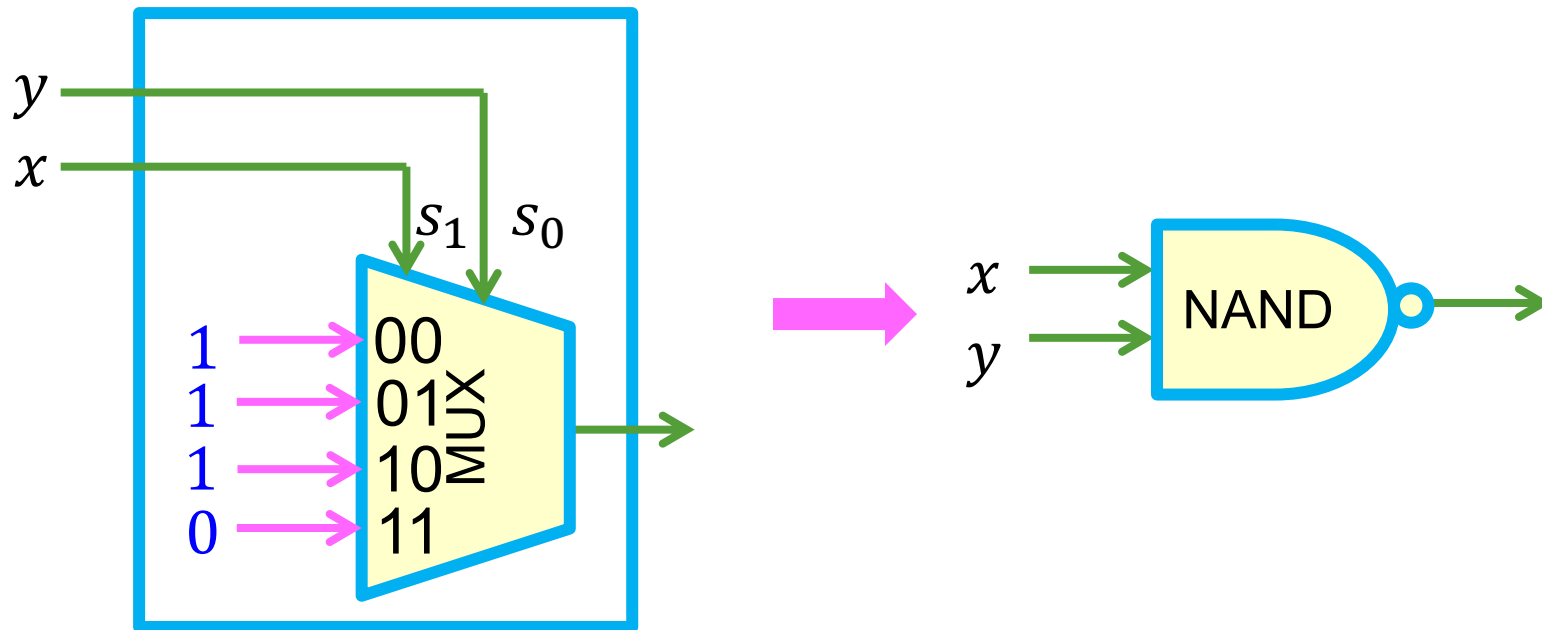- ▶ You can do **any** function of 2 vars with one 4-to-1 multiplexor (MUX).



Network Repair: Using Quantification

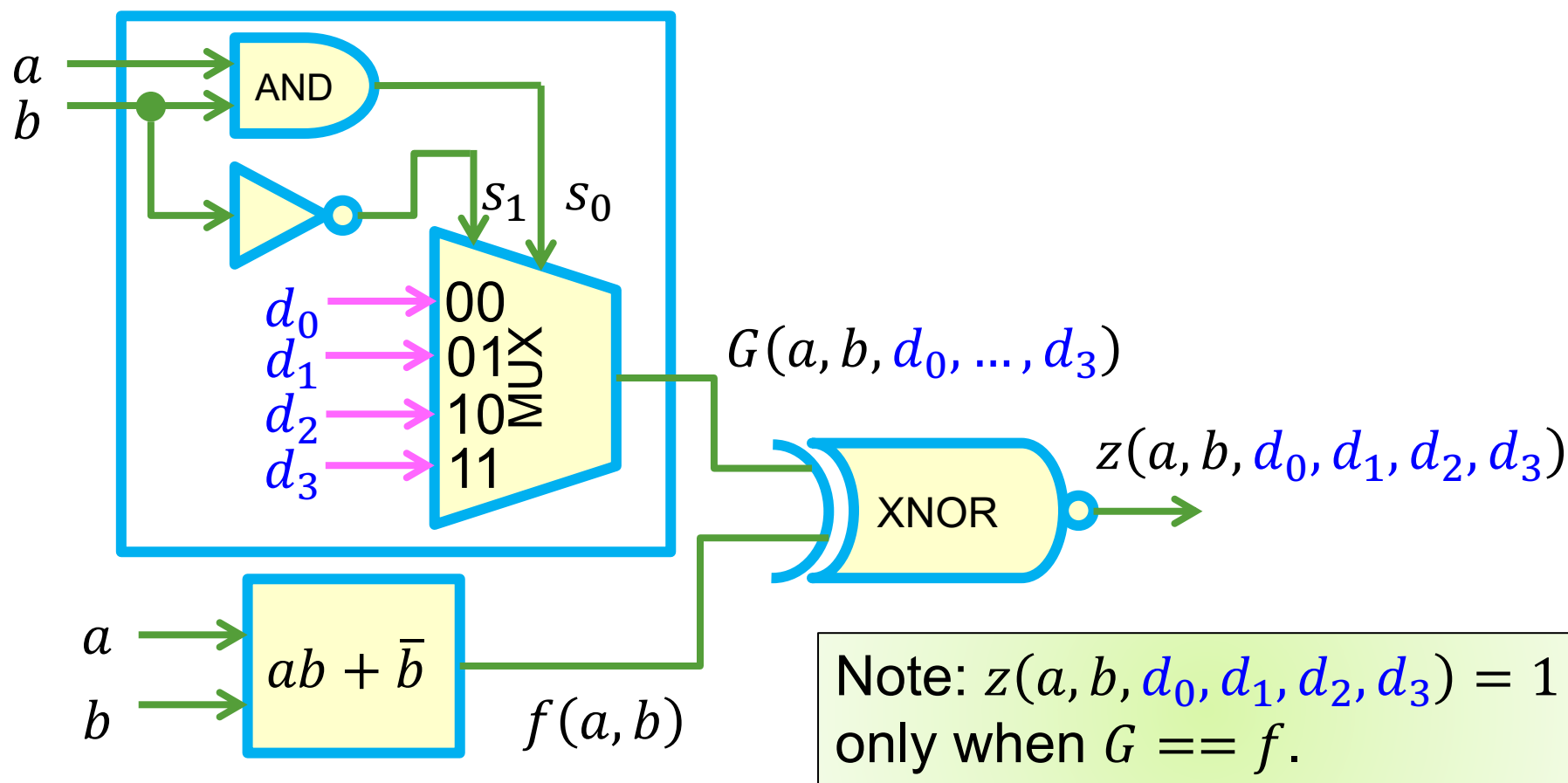- Next trick: XNOR $G(a, b, d_0, \dots, d_3)$ with the specification $f(a, b)$.



Using Quantification

► What do we need?

— Values of d_0, d_1, d_2, d_3 that make $z = 1$ **for all** possible values of inputs a, b .

— They are values of d_0, d_1, d_2, d_3 that let

$$(\forall ab \ z)(d_0, d_1, d_2, d_3) = 1$$


— The above equation is **universal quantification** of function z with respect to a, b !

— Any pattern of (d_0, d_1, d_2, d_3) that makes

$$(\forall ab \ z)(d_0, d_1, d_2, d_3) = 1$$

will do it!

Network Repair via Quantification

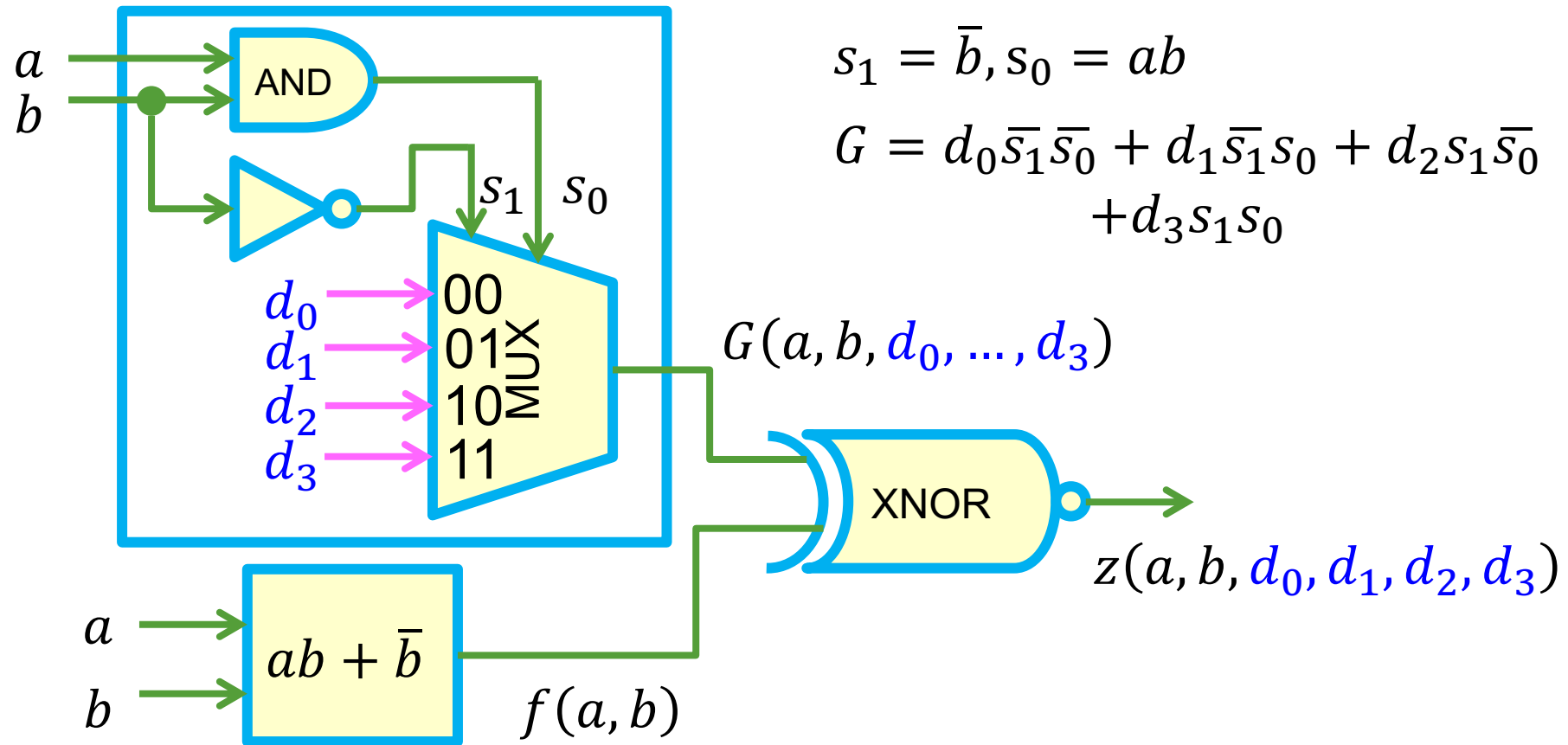

Network Repair via Quantification

➤ As a result

$$- G(a, b, d_0, \dots, d_3) = d_0 \bar{a}b + d_1 ab + d_2 \bar{b}$$

$$- f(a, b) = ab + \bar{b}$$

$$- z(a, b, d_0, \dots, d_3) = G(a, b, d_0, \dots, d_3) \bar{\oplus} f(a, b)$$

➤ We want to get

$$\begin{aligned} & (\forall ab \ z)(d_0, d_1, d_2, d_3) \\ & = Z_{\bar{a}\bar{b}} \cdot Z_{\bar{a}b} \cdot Z_{a\bar{b}} \cdot Z_{ab} \end{aligned}$$

➤ To simplify the computation, we will apply the relation:

$$Z_{ab} = G_{ab} \bar{\oplus} f_{ab}$$

Network Repair via Quantification

- $G(a, b, d_0, \dots, d_3) = d_0 \bar{a}b + d_1 ab + d_2 \bar{b}$
- $f(a, b) = ab + \bar{b}$
- $z(a, b, d_0, \dots, d_3) = G(a, b, d_0, \dots, d_3) \bar{\oplus} f(a, b)$
- $z_{\bar{a}\bar{b}} = G_{\bar{a}\bar{b}} \bar{\oplus} f_{\bar{a}\bar{b}} = d_2 \bar{\oplus} 1 = d_2$
- $z_{\bar{a}b} = G_{\bar{a}b} \bar{\oplus} f_{\bar{a}b} = d_0 \bar{\oplus} 0 = \bar{d_0}$
- $z_{a\bar{b}} = G_{a\bar{b}} \bar{\oplus} f_{a\bar{b}} = d_2 \bar{\oplus} 1 = d_2$
- $z_{ab} = G_{ab} \bar{\oplus} f_{ab} = d_1 \bar{\oplus} 1 = d_1$
- $(\forall ab z)(d_0, d_1, d_2, d_3) = z_{\bar{a}\bar{b}} \cdot z_{\bar{a}b} \cdot z_{a\bar{b}} \cdot z_{ab} = \bar{d_0} d_1 d_2$



Network Repair via Quantification

- Finally, we obtain $(\forall ab z)(d_0, d_1, d_2, d_3) = \overline{d_0}d_1d_2$
- To repair, we should find values of d_0, d_1, d_2, d_3 so that
$$(\forall ab z)(d_0, d_1, d_2, d_3) = 1$$
 - Not hard: $d_0 = 0, d_1 = 1, d_2 = 1, d_3 = X$ (don't care)

Network Repair

► Does $d_0 = 0, d_1 = 1, d_2 = 1, d_3 = X$ work?

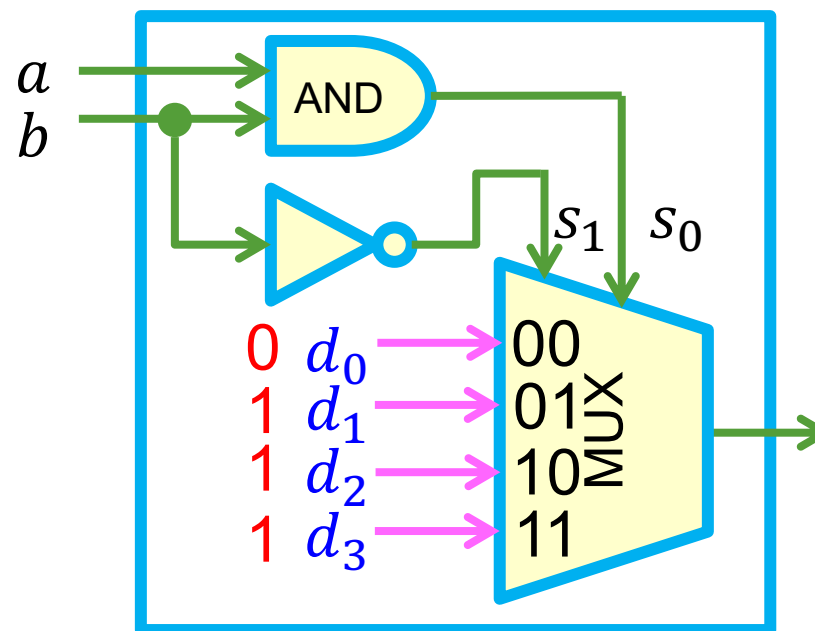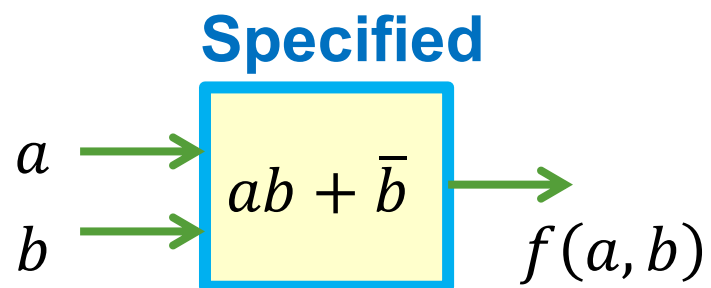— Case 1: $d_0 = 0, d_1 = 1, d_2 = 1, d_3 = 1$





MUX is an OR gate. Expected!

Network Repair

► Does $d_0 = 0, d_1 = 1, d_2 = 1, d_3 = X$ work?

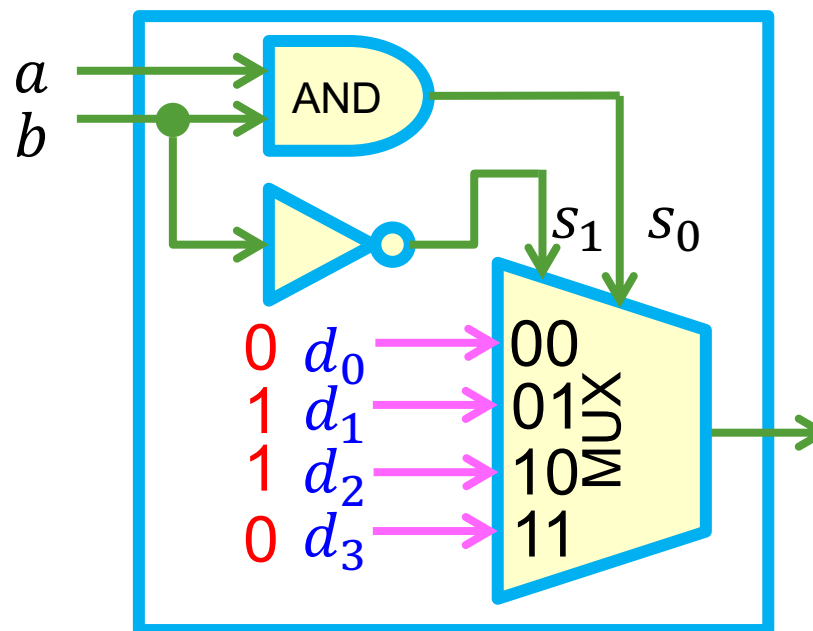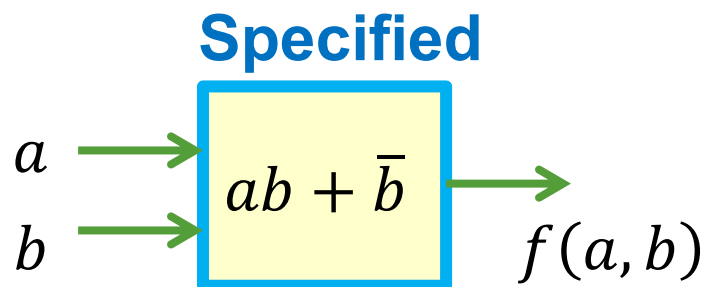— Case 2: $d_0 = 0, d_1 = 1, d_2 = 1, d_3 = 0$





MUX is an XOR gate.
Unexpected but works!

Network Repair: Summary

- This example is **tiny**...
 - But in a real example, you have a big network – 100 inputs, 50,000 gates.
 - When the design doesn't work, it is a major hassle to go through the design to fix it.
 - This gives a mechanical procedure to answer: Can we change 1 gate to repair?
- What we haven't seen yet: **Computation strategy** to mechanically find inputs to make
$$(\forall a b z)(d_0, d_1, d_2, d_3) = 1$$
 - This computation is called **Boolean Satisfiability (SAT)**.
 - We will see how to solve Boolean SAT problem efficiently later.



Representation of Combinational Circuits

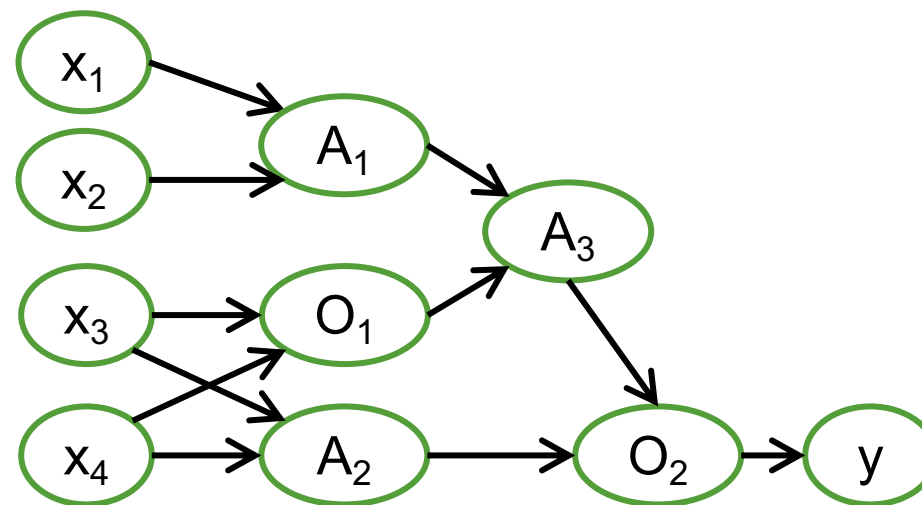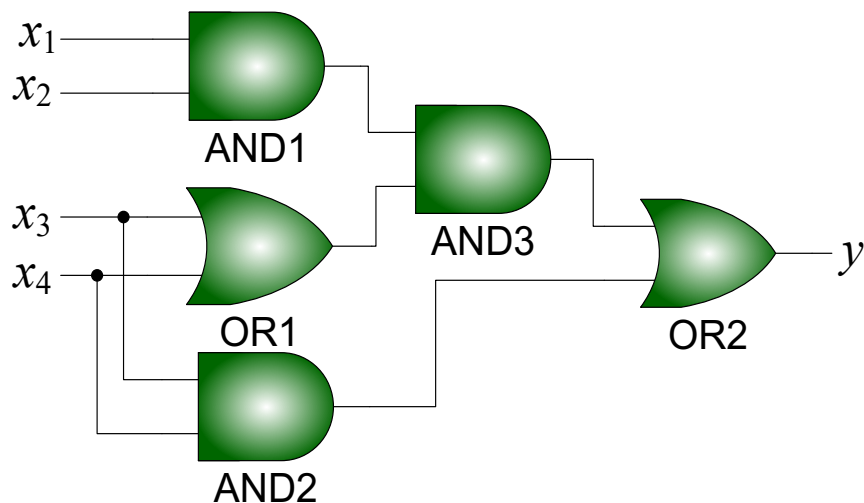- Represented as a directed graph.
 - Inputs, outputs, and gates ➔ nodes
 - Wires ➔ directed edges.
 - Why directed edges? Signal flow has direction.




Representation of Combinational Circuits

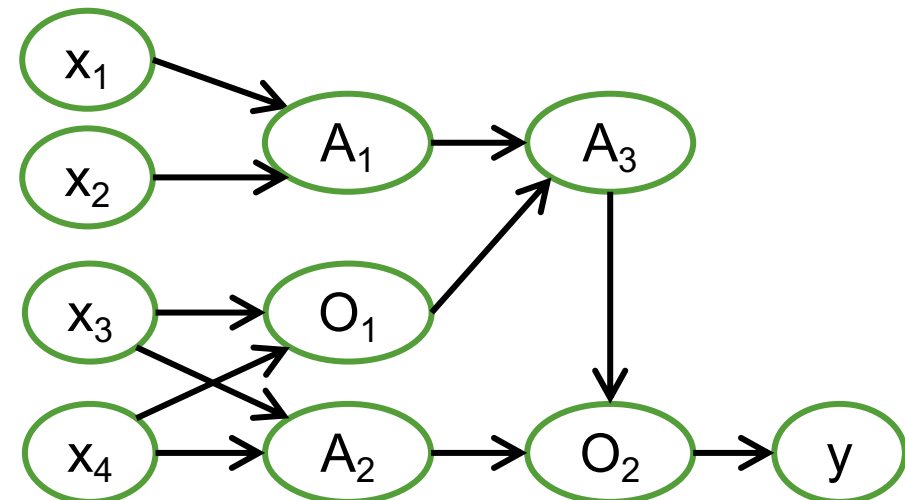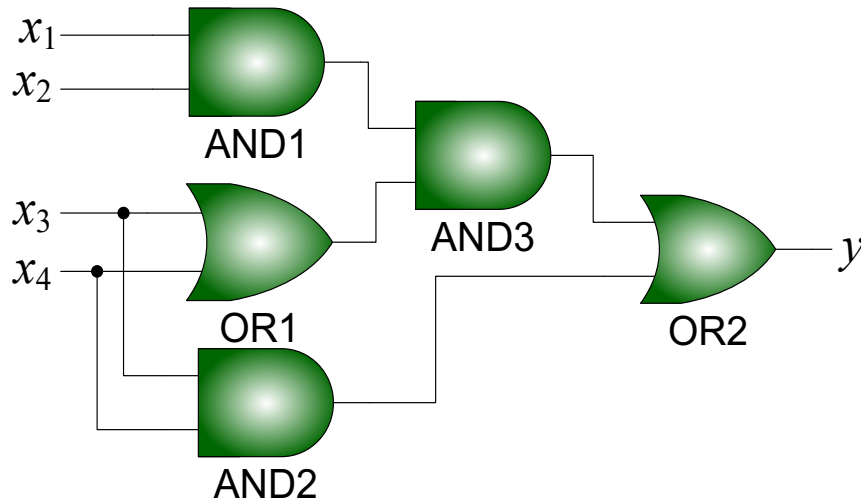- ▶ Since a combinational circuit has no loops, the corresponding graph is a **directed acyclic graphs (DAG)**.
 - DAG: A directed graph with no cycles.



Traversal of Combinational Circuits

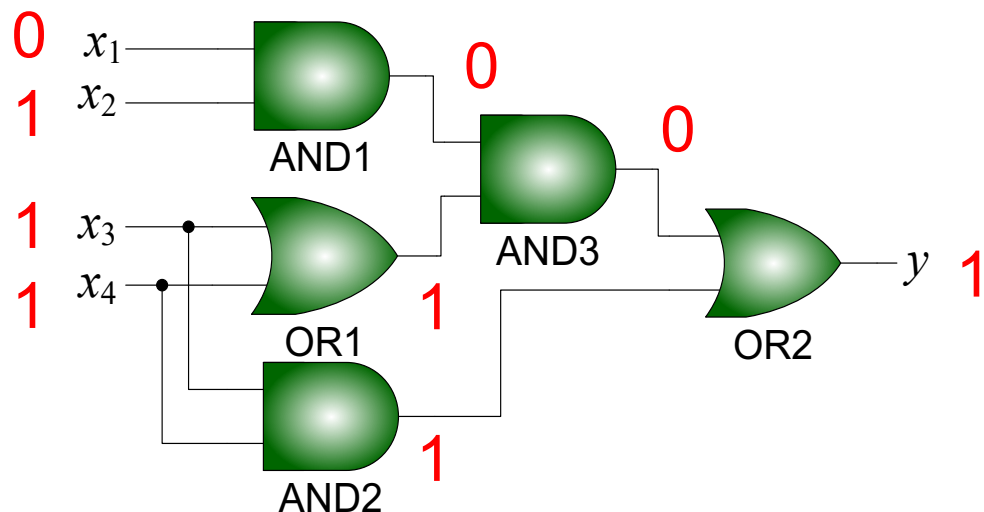- Many operations on combinational circuit need to traverse it.
- Example: obtain the output given an input pattern.




How to approach this kind of traversal as a computation?

Answer: Topological Sorting.


Topological Sorting

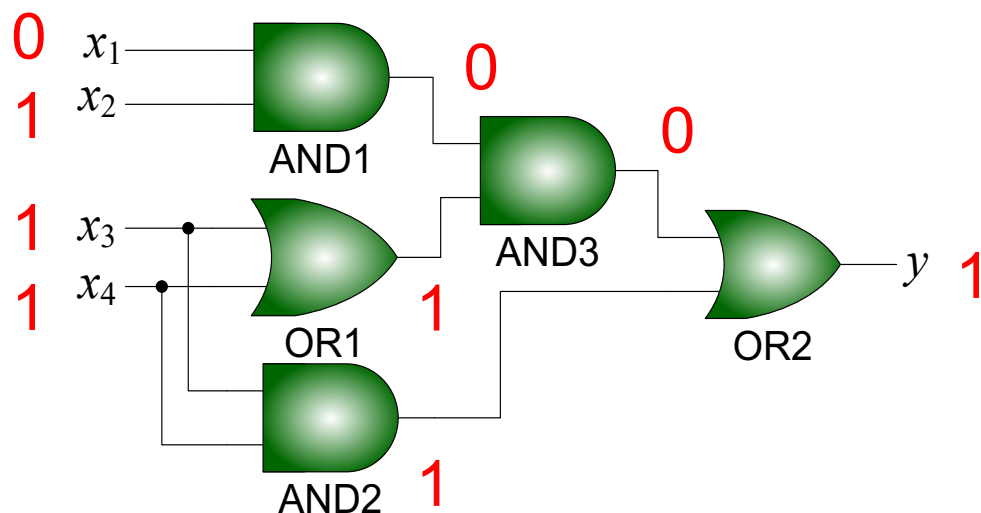- Observation on computing the output of a combinational circuit:
 - The output of each gate can be computed only when all of its inputs are known. ➔ We have to obtain its **inputs** before obtaining **output**.
 - In other words, if there is a wire (edge) from gate (node) u to v , then gate (node) u should be visited before gate (node) v .
 - This is exactly **topological sorting**.



One possible visiting order:
 $x_1, x_2, x_3, x_4, \text{AND1}, \text{OR1},$
 $\text{AND2}, \text{AND3}, \text{OR2}, y.$

Topological Sorting

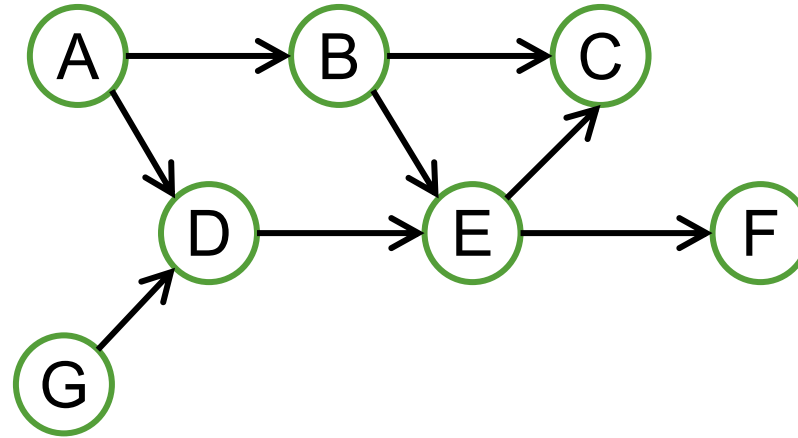

- Topological sorting is not necessarily unique:
 - A, G, D, B, E, C, F and A, B, G, D, E, F, C are both topological sorting.
- Are the following orderings topological sorting?
 - A, B, E, G, D, C, F
 - A, G, B, D, E, F, C


Topological Sorting: Algorithm

➤ Based on a **queue**.

➤ Algorithm:

1. Compute the in-degrees of all nodes. (**in-degree**: number of **incoming** edges of a node.)
2. Enqueue all in-degree 0 nodes into a queue.
3. While queue is not empty
 1. Dequeue a node v from the queue and visit it.
 2. Decrement in-degrees of node v 's neighbors.
 3. If any neighbor's in-degree becomes 0, enqueue it into the queue.

Topological Sorting Algorithm: Example

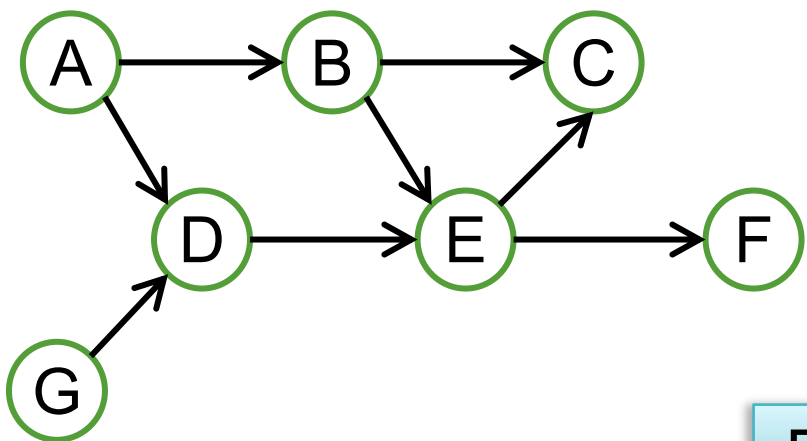

Queue

Enqueue A and G


In-degrees

| | | | | | | |
|---|---|---|---|---|---|---|
| A | B | C | D | E | F | G |
| 0 | 1 | 2 | 2 | 2 | 1 | 0 |

Order

| | | | | | | |
|--|--|--|--|--|--|--|
| | | | | | | |
|--|--|--|--|--|--|--|

Topological Sorting Algorithm: Example

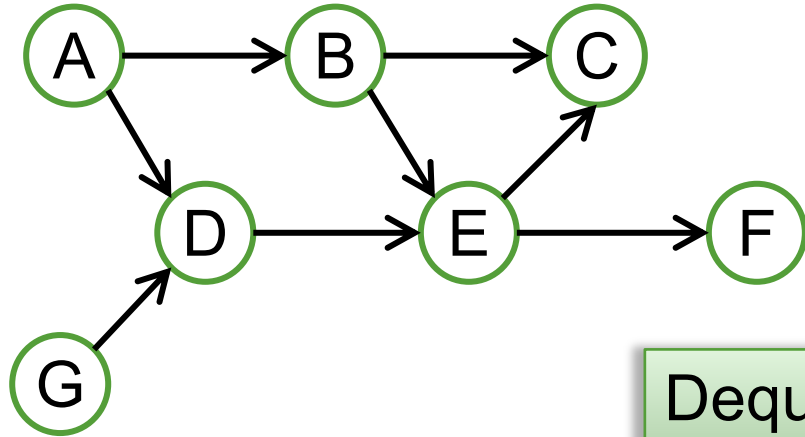

Queue

| |
|---|
| A |
| G |

Dequeue A, visit A, and decrement in-degrees of A's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 1 | 2 | 2 | 2 | 1 | 0 |

Order

| | | | | | | |
|--|--|--|--|--|--|--|
| | | | | | | |
|--|--|--|--|--|--|--|

Topological Sorting Algorithm: Example

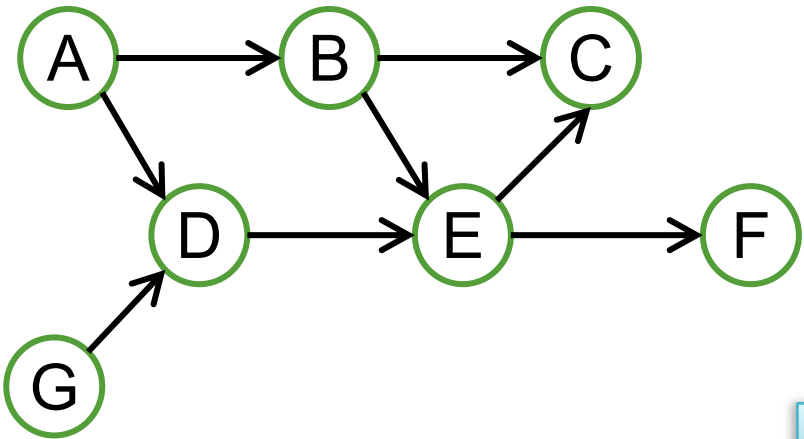

Queue

G

Enqueue B


In-degrees

| A | B | C | D | E | F | G |
|---|-----|---|-----|---|---|---|
| 0 | 1 0 | 2 | 2 1 | 2 | 1 | 0 |

Order

| | | | | | | |
|---|--|--|--|--|--|--|
| A | | | | | | |
|---|--|--|--|--|--|--|

Topological Sorting Algorithm: Example

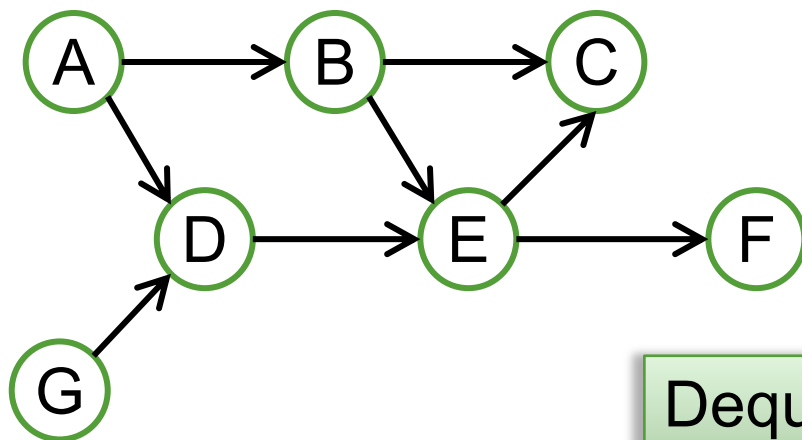

Queue

| |
|---|
| G |
| B |

Dequeue G, visit G, and decrement in-degrees of G's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 2 | 1 | 2 | 1 | 0 |

Order

| | | | | | | |
|---|--|--|--|--|--|--|
| A | | | | | | |
|---|--|--|--|--|--|--|

Topological Sorting Algorithm: Example

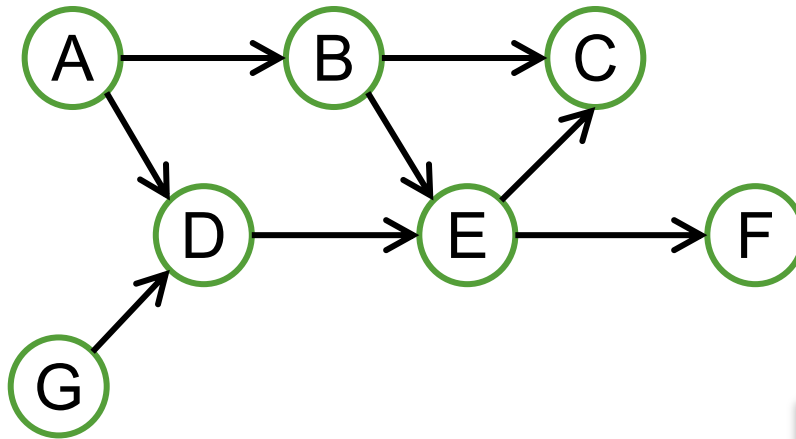

Queue

B

Enqueue D


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|-----|---|---|---|
| 0 | 0 | 2 | 4 0 | 2 | 1 | 0 |

Order

| | | | | | | |
|---|---|--|--|--|--|--|
| A | G | | | | | |
|---|---|--|--|--|--|--|

Topological Sorting Algorithm: Example

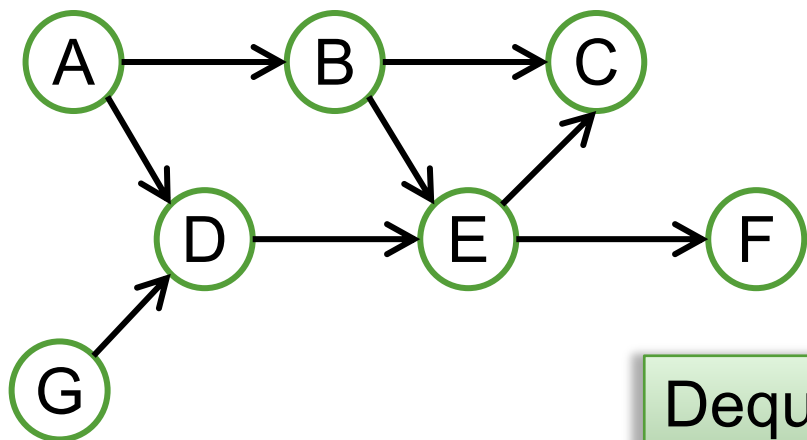

Queue

| |
|---|
| B |
| D |

Dequeue B, visit B, and decrement in-degrees of B's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 2 | 0 | 2 | 1 | 0 |

Order

| | | | | | | |
|---|---|--|--|--|--|--|
| A | G | | | | | |
|---|---|--|--|--|--|--|

Topological Sorting Algorithm: Example

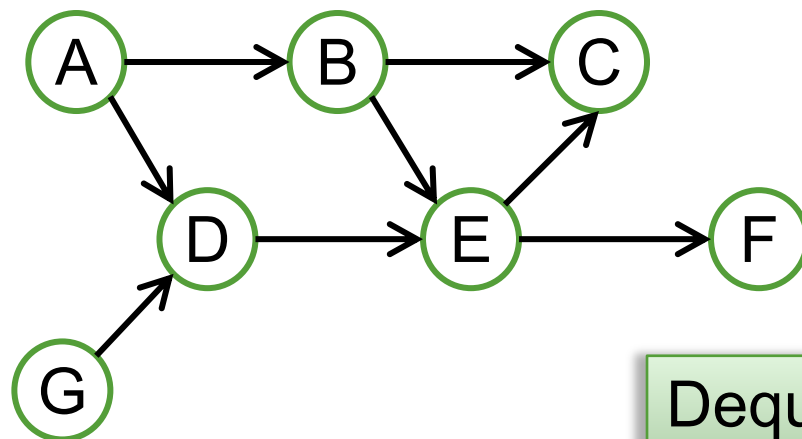

Queue

D

Dequeue D, visit D, and decrement in-degrees of D's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 2 | 0 | 2 | 1 | 0 |

Order

| | | | | | | |
|---|---|----------|--|--|--|--|
| A | G | B | | | | |
|---|---|----------|--|--|--|--|

Topological Sorting Algorithm: Example

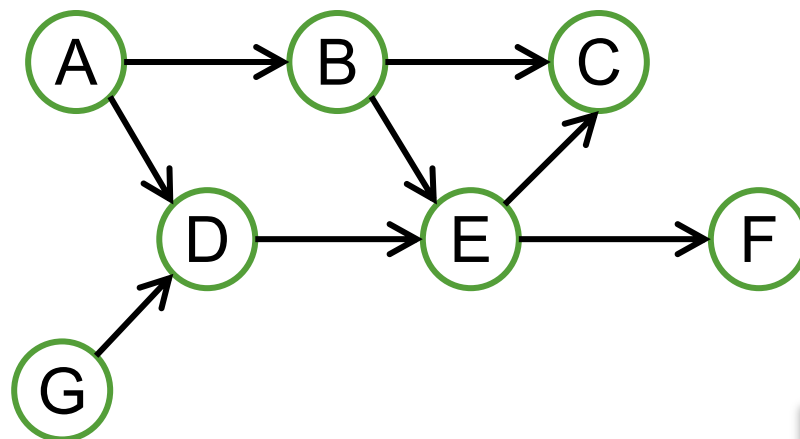

Queue

Enqueue E


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|-----|---|---|
| 0 | 0 | 1 | 0 | 4 0 | 1 | 0 |

Order

| | | | | | | |
|---|---|---|---|--|--|--|
| A | G | B | D | | | |
|---|---|---|---|--|--|--|

Topological Sorting Algorithm: Example

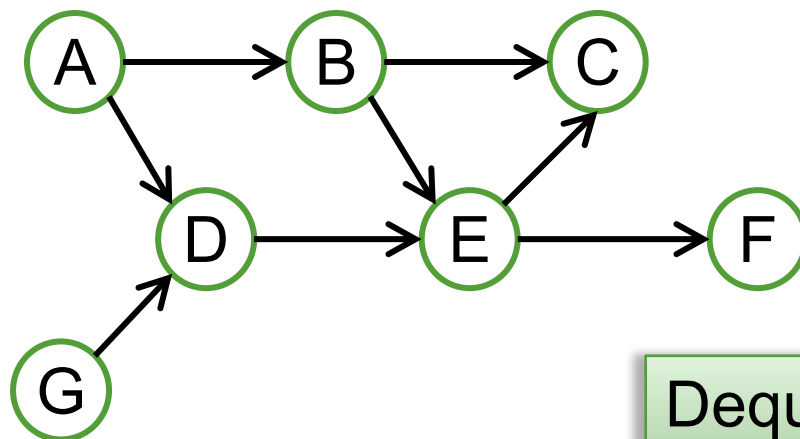

Queue

E

Dequeue E, visit E, and decrement in-degrees of E's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |

Order

| | | | | | | |
|---|---|---|---|--|--|--|
| A | G | B | D | | | |
|---|---|---|---|--|--|--|

Topological Sorting Algorithm: Example

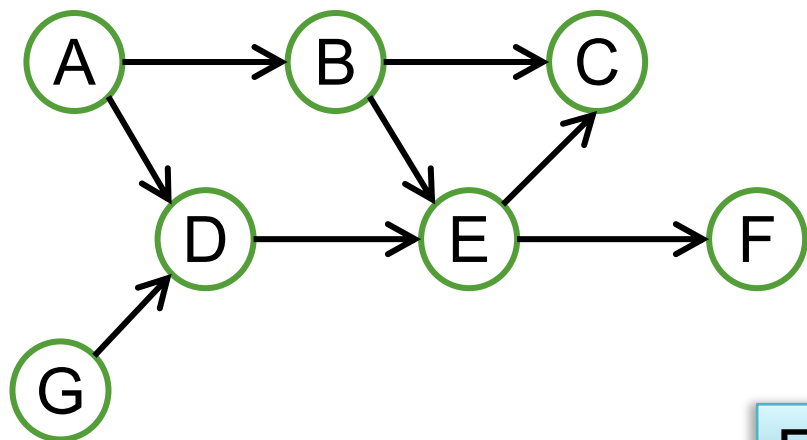

Queue

Enqueue C and F


In-degrees

| | | | | | | |
|---|---|-----|---|---|-----|---|
| A | B | C | D | E | F | G |
| 0 | 0 | 1 0 | 0 | 0 | 1 0 | 0 |

Order

| | | | | | | |
|---|---|---|---|---|--|--|
| A | G | B | D | E | | |
|---|---|---|---|---|--|--|

Topological Sorting Algorithm: Example

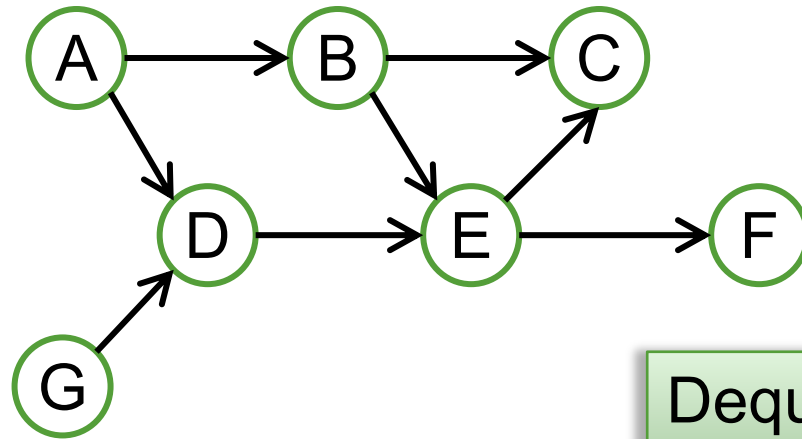

Queue

| |
|---|
| C |
| F |

Dequeue C, visit C, and decrement in-degrees of C's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |

Order

| | | | | | | |
|---|---|---|---|---|--|--|
| A | G | B | D | E | | |
|---|---|---|---|---|--|--|

Topological Sorting Algorithm: Example

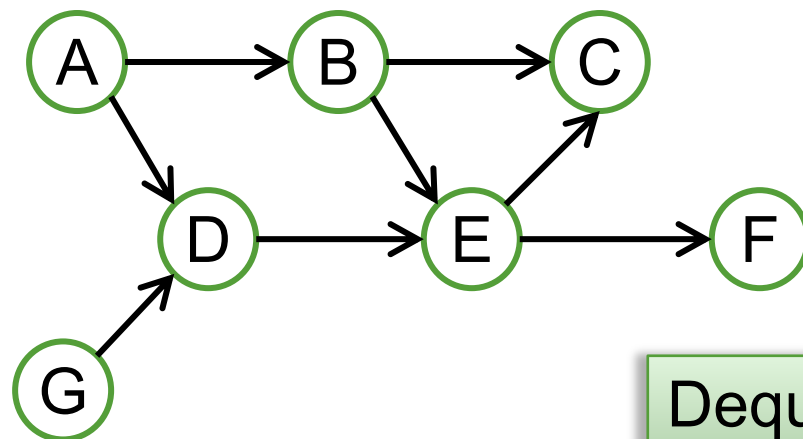

Queue

F

Dequeue F, visit F, and decrement in-degrees of F's neighbors.


In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |

Order

| | | | | | | |
|---|---|---|---|---|---|--|
| A | G | B | D | E | C | |
|---|---|---|---|---|---|--|

Topological Sorting Algorithm: Example

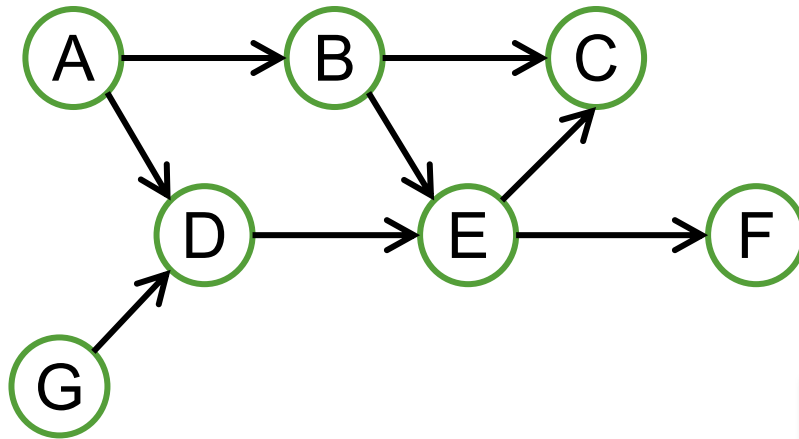

Queue

Queue is now empty. Done!

In-degrees

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |

Order

| | | | | | | |
|---|---|---|---|---|---|----------|
| A | G | B | D | E | C | F |
|---|---|---|---|---|---|----------|

Circuit Netlist Format

- We also need to store circuits as a text file.
 - ... to be processed by different programs, e.g., layout synthesis tool, SPICE, schematic viewer, etc.
 - Such files essentially store a netlist of gates.

- Many formats exist:
 - Berkeley Logic Interchange Format (BLIF)
 - Structured Verilog Format
 - Benchmark Format

Example: Benchmark Format

```
INPUT(x1)
INPUT(x2)
INPUT(x3)
INPUT(x4)
OUTPUT(y)
g1=AND(x1,x2)
g2=OR(x3,x4)
g3=AND(x3,x4)
g4=AND(g1,g2)
y=OR(g3,g4)
```

