



《芯片设计自动化与智能优化》 Static Timing Analysis

The slides are partly based on the lecture notes of Prof. David Z. Pan at UT Austin and Prof. Tsung-Wei Huang at UW Madison.


Yibo Lin

Peking University

How Fast A Chip Can Run?



 
Technology: 5nm
Max. CPU clock: 3.2GHz
L2 cache: 12MB
Transistors: 16 billion




Technology: 32nm
Max. CPU clock: 3.3GHz (3.9GHz w. Turbo)
L2 cache: 15MB

Maximum Clock Frequency


Combinational logic

 


Sequential logic

 

Timing paths

 


Timing Arc

 


Timing Arc and Timing Graph

 - Timing arc can be categorized to cell arc or net arc




Timing Arc and Timing Graph

 

7 Timing Graph

 - Timing graph consists of pins and timing arcs
- Given the delay of each timing arc, we can derive the path delays





Net Delay

- Ignoring interconnects
- Lumped capacitance model
- RC tree model
- RLC tree model
- Transmission line models (RC, LC, RLC)
- RC/RLC network


Interconnect Models as a Capacitor

Ignoring interconnects

  

$$V_{\text{out}}(t) = V_{\text{DD}} (1 - e^{-t/T})$$

Lumped capacitance model

 

$$T = R_d (C_{\text{output}} + C_1 + C_2 + C_3)$$

or

$$T = R_d (C_{\text{output}} + C_1 + C_2 + C_3 + C_{\text{wire}})$$

$$V_{\text{out}}^{-1}(0.5V_{\text{DD}}) = (\ln 2) T = 0.693 T$$

$$V_{\text{out}}(T) = 0.632 V_{\text{DD}}$$

Analysis of Simple RC Circuit

$$\rightarrow R \cdot i(t) + v(t) = v_T(t)$$


$$\rightarrow i(t) = \frac{d(Cv(t))}{dt} = C \frac{dv(t)}{dt}$$

$$\rightarrow RC \frac{dv(t)}{dt} + v(t) = v_T(t)$$

State variable

Input waveform

 First-order linear differential equation
with constant coefficients



Analysis of Simple RC Circuit

► Zero-input response (natural response)

- $RC \frac{dv(t)}{dt} + v(t) = 0 \Rightarrow v(t) = K e^{-\frac{t}{RC}}$

► Step-input response

- $RC \frac{dv(t)}{dt} + v(t) = v_0 u(t) \Rightarrow v(t) = K e^{-\frac{t}{RC}} + v_0 u(t)$

- Match initial state


- $v(0) = 0 \Rightarrow K + v_0 u(t) = 0$

- Output response for step-input

- $v(t) = v_0 (1 - e^{-\frac{t}{RC}}) u(t)$

► You can get same result by Laplace Transform

 - Try google it (“RC circuit Laplace Transform”)





Delays of Simple RC Circuit

- $v(t) = v_0(1 - e^{-t/RC})$
 - Waveform under step input $v_0u(t)$
- $v(t) = 0.5v_0 \Rightarrow t = 0.7RC$
 - i.e., *delay* = $0.7RC$ (50% delay)
- $v(t) = 0.1v_0 \Rightarrow t = 0.1RC$
- $v(t) = 0.9v_0 \Rightarrow t = 2.3RC$
 - i.e., *rise time* = $2.2RC$ (if defined as time from 10% to 90% of Vdd)
- Commonly used metric
 - $T_D = RC$ (Elmore delay)


Interconnect Models as a Tree

  - RC tree
- RLC tree
- Transmission line models (RC, LC, RLC)



Interconnect Models as a Tree

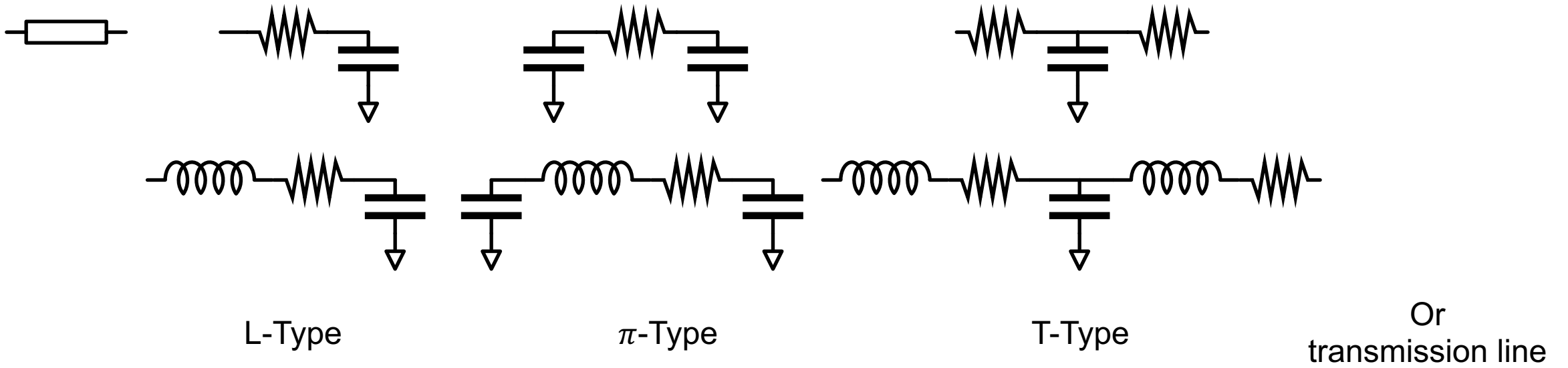- RC tree
- RLC tree
- Transmission line models (RC, LC, RLC)



Determining Which Model to Use

- Some rule-of-thumbs
- Need to consider C
 - if interconnect C is comparable to C of gates driven
- Need to consider R
 - if interconnect R is comparable to R of driver
- Need to consider L
 - if ωL is comparable to R of interconnect

More Interconnects as RC Trees

- Each wire maybe segmented into several edges
- Each edge E modeled as a π -type or L -type circuit
- $r_E = \text{unit res.} \times \text{length}(E)$
- $c_E = \text{unit cap.} \times \text{length}(E)$

Elmore Delay for RC Tree

Definition



- $H(t)$ = step response
- $h(t)$ = impulse response = rate of change of $H(t)$
- $T_{50\%}$ = median of $h(t)$

Elmore delay [Elmore, 1948]


- $T_D = \text{mean of } h(t) = \int_0^\infty h(t) \cdot t \cdot dt$
- Approximates the median of $h(t)$ by mean

Computation: $T_D(s_o, s_i) = \sum_{\text{node } k \text{ in } \text{src-to-sink path}} R_k \cdot \text{Cap}(k)$

- [Rubinstein et al, TCAD 1983]

  


Basic Input Waveform

 

unit step function
 
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$



unit impulse function


$$\delta(t) : P_T(t) \quad \text{when } T \rightarrow 0$$

$$\delta(t) = \begin{cases} 0 & \text{for } t \neq 0 \\ \text{singular} & \text{for } t = 0 \end{cases}$$

$$\text{s.t. } \forall \zeta > 0, \int_{-\zeta}^{\zeta} \delta(t) dt = 1$$


Elmore Delay for Monotonic Responses

 - [Elmore, J. App. Phy. 1948]
- Assumptions
 - Unit step input
 - Monotone output response
 - $v(t)$: output response (monotone)
 - $v'(t)$: rate of change of $v(t)$
- Basic idea
 - Use mean of $v'(t)$ to approximate median of $v'(t)$



Elmore Delay for Monotonic Responses

 - $T_{50\%}$: median of $v'(t)$, since
 - $\int_0^{T_{50\%}} v'(t) dt = \int_{T_{50\%}}^{+\infty} v'(t) dt$
 - Half of final value of $v(t)$
- Elmore delay $T_D = \text{mean of } v'(t)$
 - $T_D = \int_0^{\infty} t v'(t) dt$




Elmore Delay for Monotonic Responses

Definition

- $h(t)$ = impulse response
- T_D = mean of $h(t) = \int_0^\infty h(t) \cdot t \cdot dt$

Interpretation

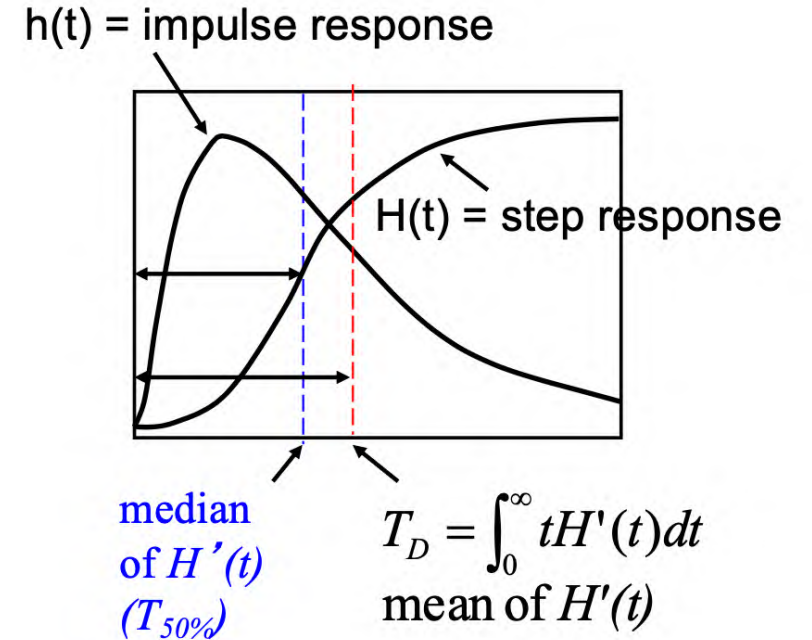- $H(t)$ = output of response (step response)
- $h(t)$ = rate of change of $H(t)$
- $T_{50\%}$ = median of $h(t)$
- Elmore delay approximates the median of $h(t)$ by the mean of $h(t)$



Elmore Delay of a RC Tree [Rubinstein et al, TCAD'83]


P_i : path from input to node i ; S_i : subtree rooted at i

R_{jk} : resistance of common path

$P_j \cap P_k$ from input to j & k

Theorem : Elmore delay to node i

$$T_{D_i} = \sum_k R_{ki} C_k$$

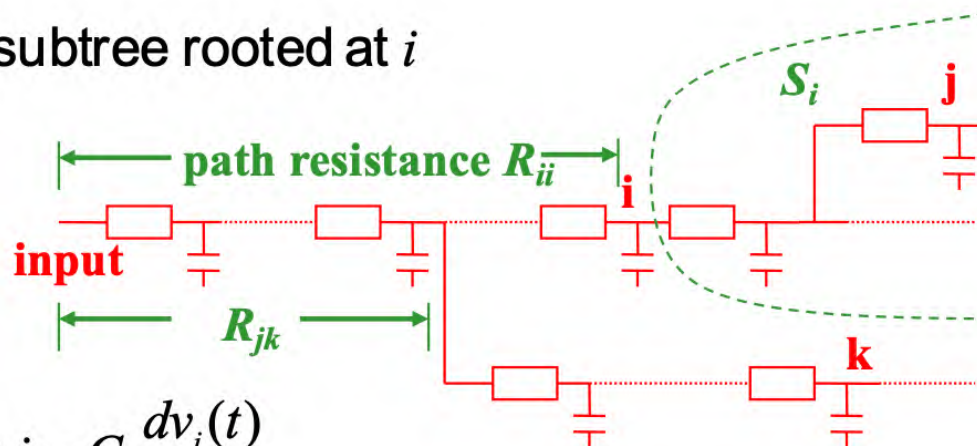

Proof : The current to cap. of node $i = C_i \frac{dv_i(t)}{dt}$

$1 - v_i(t)$ = The voltage drop on $P_i = \sum_{k \in P_i} R_k \cdot (\text{current to all cap's in } S_k)$

$$= \sum_k (\text{current to cap } k) \cdot (\text{common path res. between } P_i \text{ and } P_k)$$

$$= \sum_k C_k \frac{dv_k(t)}{dt} \cdot R_{ki} = \sum_k R_{ki} C_k \frac{dv_k(t)}{dt}$$

$$T_{D_i} = \int_0^\infty v'_i(t) t \cdot dt = v_i(t) \cdot t \Big|_0^\infty - \int_0^\infty v_i(t) dt$$

$$= \lim_{T \rightarrow \infty} [v_i(T) \cdot T - \int_0^T v_i(t) dt] = \lim_{T \rightarrow \infty} (v_i(T) - 1) \cdot T + \int_0^\infty (1 - v_i(t)) dt$$

Elmore Delay of a RC Tree [Rubinstein et al, TCAD'83]

We can show that $\lim_{T \rightarrow \infty} (1 - v_i(T)) \cdot T = 0$


i.e. $1 - v_i(T)$ goes to 0 at a much faster rate than $1/T$ when $T \rightarrow \infty$

Let $f_i(t) = \int_0^t [1 - v_i(x)] dx$


$$\begin{aligned} f_i(t) &= \int_0^t \sum_k R_{ki} C_k \frac{dv_k(x)}{dx} dx \\ &= \sum_k R_{ki} C_k v_k(t) \\ &= \sum_k R_{ki} C_k - \sum_k R_{ki} C_k [1 - v_k(t)] \quad (1) \end{aligned}$$

$$f_i(\infty) = \sum_k R_{ki} C_k$$
 
$$\begin{aligned} \therefore T_{Di} &= \lim_{T \rightarrow \infty} (1 - v_i(T))T + \int_0^\infty [1 - v_i(t)] dt \\ &= f_i(\infty) = \sum_k R_{ki} C_k \end{aligned}$$




Elmore Delay: Example

 

Elmore Delay: Example

Elmore delay model

 - $R_{S \rightarrow A} = R_1(C_1 + C_2 + \dots + C_6) + R_2C_2$
- $R_{S \rightarrow B} = R_1(C_1 + C_2 + \dots + C_6) + R_3(C_3 + C_4 + C_5 + C_6) + R_4C_4$
- $R_{S \rightarrow C} = R_1(C_1 + C_2 + \dots + C_6) + R_3(C_3 + C_4 + C_5 + C_6) + R_5(C_5 + C_6) + R_6C_6$
- Essentially dynamic programming!



Elmore Delay: Example


Elmore delay model

— Compute load for each node

- $L_A = C_2, L_B = C_4, L_C = C_6$
- $L_{M_3} = C_5 + L_C$
- $L_{M_2} = C_3 + L_{M_3} + L_B$
- $L_{M_1} = C_1 + L_{M_2} + L_A$


— Compute delay

- $D_{S \rightarrow M_1} = R_1 L_{M_1}$
- $D_{S \rightarrow A} = D_{S \rightarrow M_1} + D_{M_1 \rightarrow A}$
- $D_{S \rightarrow B} = D_{S \rightarrow M_2} + D_{M_2 \rightarrow B} = D_{S \rightarrow M_1} + D_{M_1 \rightarrow M_2} + D_{M_2 \rightarrow B} = D_{S \rightarrow M_1} + R_3 L_{M_2} + D_{M_2 \rightarrow B}$
- $D_{S \rightarrow C} = D_{S \rightarrow M_3} + D_{M_3 \rightarrow C} = D_{S \rightarrow M_2} + D_{M_2 \rightarrow M_3} + D_{M_3 \rightarrow C} = D_{S \rightarrow M_2} + R_5 L_{M_3} + D_{M_3 \rightarrow C}$

 

Bottom-up traversal

Tree Representation

 

Top-down traversal

Elmore Delay: Example

Elmore delay model

— Compute β for each node

- $\beta_{M_1} = R_1(C_1d_1 + C_2d_2 + C_3d_3 + C_4d_4 + C_5d_5 + C_6d_6)$
- $\beta_A = \beta_{M_1} + R_2C_2d_2$
- $\beta_{M_2} = \beta_{M_1} + R_3(C_3d_3 + C_4d_4 + C_5d_5 + C_6d_6)$
- $\beta_B = \beta_{M_2} + R_4C_4d_4$


— Compute output slew

- $s_A \approx \sqrt{s_S^2 + \hat{s}_A^2} = \sqrt{s_S^2 + 2\beta_A^2 + d_A^2}$
- $(\hat{s}_A \approx \sqrt{2\beta_A - d_A^2})$

Bottom-up traversal

Top-down traversal

Tree Representation

 

Properties of Elmore Delay

► Advantages


- Simple closed-form expression
 - Useful for interconnect optimization
- Upper bound of 50% delay [Gupta et al, 97]
 - Actual delay asymptotically approaches Elmore delay as input signal rise time increases
- High fidelity [Boese et al., 93],[Cong-He,96]
 - Good solutions under Elmore delay are good solutions under actual (SPICE) delay

► Disadvantages

- Low accuracy, no waveform information
- Inherently cannot handle inductance effect

Insights on Elmore Delay

 - ▶ Why Elmore delay is an upper bound of 50% signal delay for RC tree?
 - What is an upper bound
 - Analyze one R and C network
- ▶ When is the mean equal to the median



More Accurate Delay Models with Higher Order Moments

- Applicable to general RLC networks
- Used for waveform approximation (e.g. Asymptotic Waveform Evaluation (AWE))
- More accurate than Elmore delay
- Much more computational intensive than Elmore delay model too!

Transfer Function of Interconnect Network

- Each RC/RLC network transforms the input signal into an output signal
- This transformation is characterized by a “transfer function”
- Transfer function of RLC network can be written as a proper
- rational function (i.e., $m < n$) in frequency domain (recall Laplace?):

$$H(s) = \frac{B_m s^m + B_{m-1} s^{m-1} + \dots + B_1 s + B_0}{A_n s^n + A_{n-1} s^{n-1} + \dots + A_1 s + A_0}$$

- Benefit?
 - Once such $H(s)$ is computed, getting output is very easy – find $INP(s)$,
 - find $H(s) * INP(s)$, take inverse Laplace transform = output waveform
- Thus, serves like “signature” of an interconnect network

Moments of Impulse Response $h(t)$

- Definition of moments

$$h(t) \xrightarrow{L} H(s)$$

$$e^x = \sum_{i=0}^{\infty} \frac{1}{i!} x^i$$

$$\begin{aligned} H(s) &= \int_0^{\infty} h(t) e^{-st} dt = \int_0^{\infty} h(t) \left(\sum_{i=0}^{\infty} \frac{1}{i!} (-st)^i \right) dt \\ &= \sum_{i=0}^{\infty} s^i \left(\frac{(-1)^i}{i!} \int_0^{\infty} h(t) t^i dt \right) = \sum_{i=0}^{\infty} s^i m_i \end{aligned}$$

$$i\text{-th moment: } m_i = \frac{(-1)^i}{i!} \int_0^{\infty} h(t) t^i dt$$

- Note that $-m_1$ gives Elmore delay when $h(t)$ is positive voltage response of impulse input

From previous slides:

Elmore Delay [Elmore, 1948]


- $T_D = \text{mean of } h(t) = \int_0^{\infty} h(t) \cdot t dt$

Significance of Moments?

- Elmore delay is the first “moment” of transfer function.
- k -th moment is the expression which gets multiplied by s^k (where s is frequency, in Laplace).
- Each moment has information about transfer function.
- For current technology nodes (< 32nm) important to consider m_1 , m_2 , m_3 , and even more!
- Some microprocessor companies use as many as 20 moments.
 - Using infinite moments would give exact waveform.
 - But would spend too much CPU time

Distributed vs Lumped RC Lines: Analysis

Assume V_{in} is a rising step signal

 


$$V_{out}(t) \xrightarrow[\text{Transform}]{\text{Laplace}} V_{out}(s)$$


$$V_{out}(s) = \frac{1}{s \cosh \sqrt{sRC}}$$

$$\text{where } \cosh(x) = \frac{e^x + e^{-x}}{2} = 1 + \frac{x^2}{2!} + \frac{x^4}{4!} + \dots \approx \begin{cases} e^x / 2 & x \gg 1 \\ 1 + \frac{x^2}{2!} + \frac{x^4}{4!} & x \ll 1 \end{cases}$$
 
$$V_{out}(t) = \begin{cases} \operatorname{erfc} \sqrt{\frac{RC}{4t}} & t \ll RC \\ 1 - 1.366e^{-2.5359t/RC} + 0.366e^{-9.4641t/RC} & t \gg RC \end{cases}$$




$$V_{out}(t) = 1 - e^{-t/RC}$$

 


$$V_{out}(t) = 1 - e^{-t/0.5RC}$$

Gauss Error Function
 
$$\operatorname{erf} z = \frac{2}{\sqrt{\pi}} \int_0^z e^{-t^2} dt.$$



Distributed vs Lumped RC Lines: Waveform

 




Distributed vs Lumped RC Lines: Delay

Output potential range	Time elapsed (RC transmission Line Model)	Time elapsed (L-type RC Network)	Time elapsed (π -type RC Network)
0 to 90%	1.0 <i>RC</i>	2.3 <i>RC</i>	1.15 <i>RC</i>
10% to 90% (rise time)	0.9 <i>RC</i>	2.2 <i>RC</i>	1.1 <i>RC</i>
0 to 63%	0.5 <i>RC</i>	1.0 <i>RC</i>	0.5 <i>RC</i>
0 to 50% (delay)	0.4 <i>RC</i>	0.693 <i>RC</i>	0.347 <i>RC</i>
0 to 10%	0.1 <i>RC</i>	0.105 <i>RC</i>	0.105 <i>RC</i>

Cell Delay

Transition delay

  
 
- Slew fall/rise
- Typical V_{th1}/V_{th2} : 10%/90%



Cell Delay


Cell/gate delay

- Delay fall/rise
- Typical V_{th} : 50%

  


Simple Cell Model

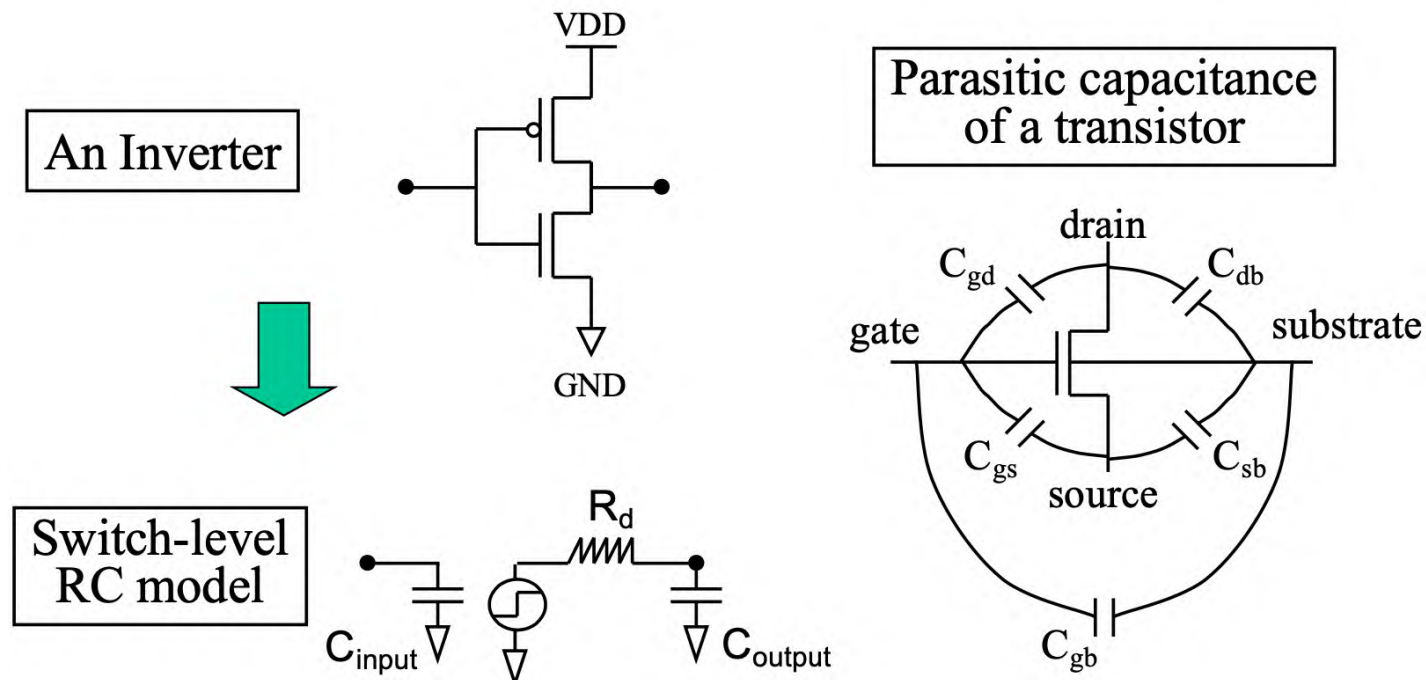- Want to model a gate by a simple RC circuit.
- Together with RC (or similar) model of interconnects, signal analysis can be done easily.



Effective Resistance

 - Model the driver by an effective linear resistance
 - Select an appropriate load C_L
 - Simulate and get 50% delay
 - Match the delay by that of an equivalent RC circuit ($R_{eff}C_L$)



- Effective resistance may depend on input slope

Driver Characterization

- Table lookup model
 - Pre-characterize driver delay and transition by
 - input transition time t_t
 - total load capacitance C_L
 - typical entry: $\{ t_t, C_L, (t_{delay}, t_{rise/fall}) \}$
- Table lookup and interpolation to obtain delay and transition time
- Can be very accurate
- Costly to create and store a multi-dimensional table

Driver Characterization

- k -factor equations for delay and output transition [Ousterhout, 1984]

- $t_{delay} = (k_1 + k_2 \cdot C_L) \cdot t_t + k_3 \cdot C_L^3 + k_4 \cdot C_L + k_5$


- $t_{fall} = (k'_1 + k'_2 \cdot C_L) \cdot t_t + k'_3 \cdot C_L^3 + k'_4 \cdot C_L + k'_5$

- Determine coefficients k_i & k'_i

- SPICE simulations for different combinations of input transition and load
 - Curve fitting by linear regression of least square fits


Cell Delay

 - Typical delay model: nonlinear delay model (NLDM)
 - Delay = f (input slew, output load)
 - Slew = g (input slew, output load)
 - f and g are nonlinear functions, usually a look-up table



Put Cells and Nets Together

 - Stage delay = delay from driver input A to loading gate C
- Two cases
 - When interconnect resistance = 0
 - When interconnect = distributed RC




When Interconnect Resistance = 0

- C_L = total interconnect capacitance + sink capacitances
- Effective resistance model
 - Stage delay = $R_{eff}C_L$
- Pre-characterized driver model
 - Compute stage delay from table lookup or k -factor equations

When Interconnect = Distributed RC

➤ Effective resistance model

 
- Augment the RC network with the effective driver resistance



➤ Compute stage delay using RC delay models

Distributed RC with Pre-characterized Driver Model

 - Compute driver delay and interconnect delay separately
- **Compute the effective capacitance seen by driver**
 - **Difficulty:** must capture shielding effect of interconnect resistance
- **Solution:**
 - Transform interconnect circuit into a π -model
 - Compute effective capacitance from π -model
- **TIP: Important! Not many people know how this is done. Must know this at least conceptually!**



Construction of π -Model

- [O'Brian-Savarino, 89]
- Bottom-up computation of first three moments of driving point admittance y_1, y_2, y_3
 - i.e., moments of response current under voltage impulse at input
 - $C_1 = \frac{y_2^2}{y_3}, C_2 = y_1 - C_1, R = -\frac{y_3^2}{y_2^3}$


Construction of π -Model

- [O'Brian-Savarino, 89]
- For an unbranched uniform distributed RC segment

- $C_1 = \frac{5C_w}{6}$

- $C_2 = \frac{C_w}{6}$

- $R = \frac{12R_w}{25}$

 


Effective Capacitance Computation

- [Qian-Pullela-Pileggi, 94]
- Transform π -model to effective capacitance model
- **Iterative computation of effective cap., t_{delay} & $t_{rise/fall}$**
 - Start with C_{eff} = total interconnect + sink capacitances
 - Get t_{delay} & $t_{rise/fall}$ from pre-characterized driver model
 - $C_{eff} = f(R, C_1, C_2, t_{delay}, t_{rise/fall})$



Open Problems for Delay Modeling

 - How to model cell/net delay accurately and efficiently
- If we are given routing of nets
 - Require **RC extraction** to get accurate RC networks
 - Require **SPICE simulation** to get accurate delay
 - Timing-consuming, e.g., current source model
- What if we are NOT given the routing
 - Pin locations only
 - E.g., in placement




Now, we have gate and wire delay


- Then what?
 - Need to be tied together to “time” the entire circuit design
- Timing:
 - **Static timing analysis (no input vector involved)**
 - Dynamic timing – very time consuming as you need to worry about input vectors/transitions, false paths, ...

Setup Time

 - A setup constraint specifies how much time is necessary for data to be available at the input of a sequential device **before** the clock edge that captures the data in the device
- This constraint enforces a **maximum** delay on the data path relative to the clock path




How to fix a setup time violation?

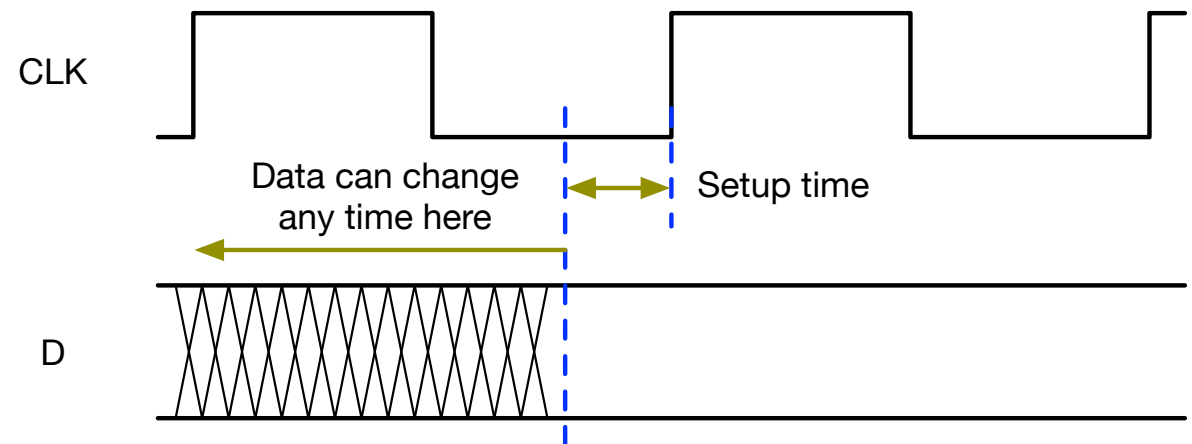


Hold Time

 - ▶ A hold constraint specifies how much time is necessary for data to be stable at the input of a sequential device **after** the clock edge that captures the data in the device
- ▶ This constraint enforces a **minimum** delay on the data path relative to the clock path



How to fix a hold time violation?

 


Arrival Time, Required Arrival Time & Slack

► Arrival time (AT)

- Each node is updated with its parents

Traversal with topological order

 

$$AT_D = \max(AT_A + 10, AT_B + 15) = 15$$

$$AT_E = AT_D + 5 = 20$$

$$AT_F = AT_E + 10 = 30$$

$$AT_G = AT_F + 5 = 35$$

$$AT_H = AT_C + 10 = 10$$


$$AT_I = \max(AT_G + 10, AT_H + 15) = 45$$

Arrival Time, Required Arrival Time & Slack

Required arrival time (RAT)

- Each node is updated by its children


Traversal with topological order

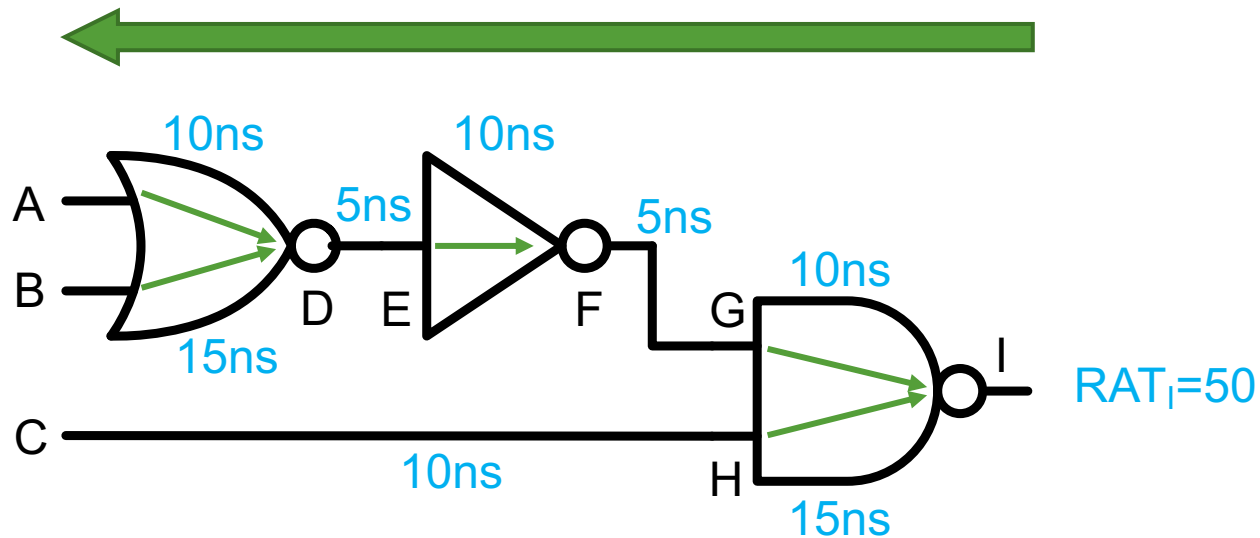

Arrival Time, Required Arrival Time & Slack


Slack

 - $Slack_i = RAT_i - AT_i$
- Critical path: $B \rightarrow D \rightarrow E \rightarrow F \rightarrow G \rightarrow I$
- **Negative** slack means timing violation!



How Does STA Determine the Frequency

 
- Given delay of timing arcs and setup/hold time of FFs
- Can you compute the maximum clock frequency?




Early/Late Modes

- In practice, the delay of a timing arc is within range
 - [early, late] or [min, max]
 - Setup analysis w. late mode & hold analysis w. early mode (exception?)


Early/Late = 5ns/15ns

 

Early/Late = 10ns/20ns

 

 - [early, late] or [min, max]
- Setup analysis w. late mode & hold analysis w. early mode (exception?)



Early/Late Modes

- In practice, the delay of a timing arc is within range

Setup tests


$$AT_D^{late} = d_{CLK:P1}^{late} + d_{clk \rightarrow Q} + d_{comb}^{late}$$

$$RAT_{setup} = RAT_D^{late} = T + d_{CLK:P2}^{early} - t_{setup}$$


Hold tests

$$AT_D^{early} = d_{CLK:P1}^{early} + d_{clk \rightarrow Q} + d_{comb}^{early}$$
 
$$RAT_{hold} = RAT_D^{early} = d_{CLK:P2}^{late} + t_{hold}$$



Graph-based Analysis

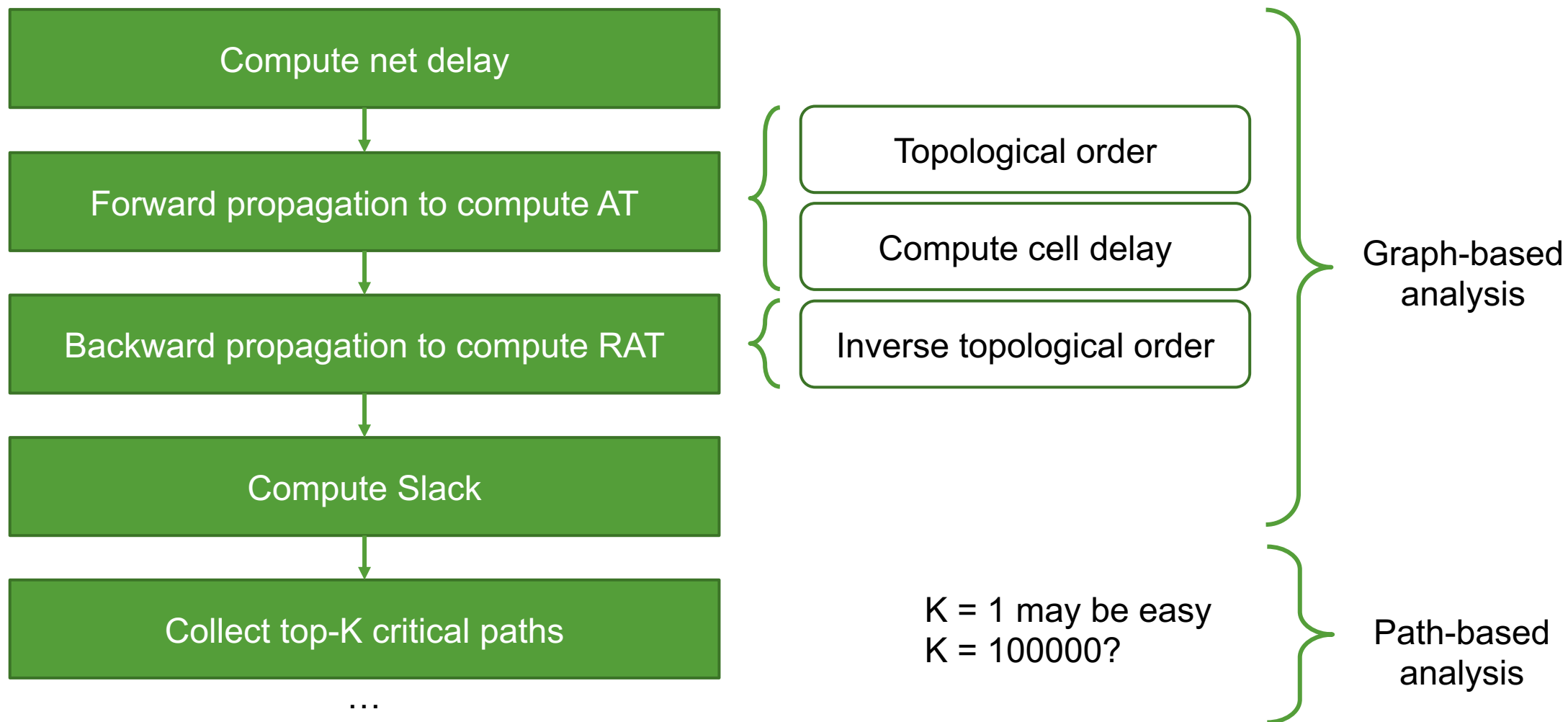


Path-based Analysis

- Given the results of graph-based analysis
- Extract top-K critical paths
- Considering common path pessimism removal (CPPR), noise, aging, ...
- Timing-consuming when K is large
 - 1~100000

Common Path Pessimism Removal (CPPR)

 
- ▶ Graph-based analysis is too pessimistic
 - In hold analysis, use P1 as early and P2 as late
 - P1 CANNOT be early and late at the same time



Common Path Pessimism Removal (CPPR)

Remove the pessimism on P1

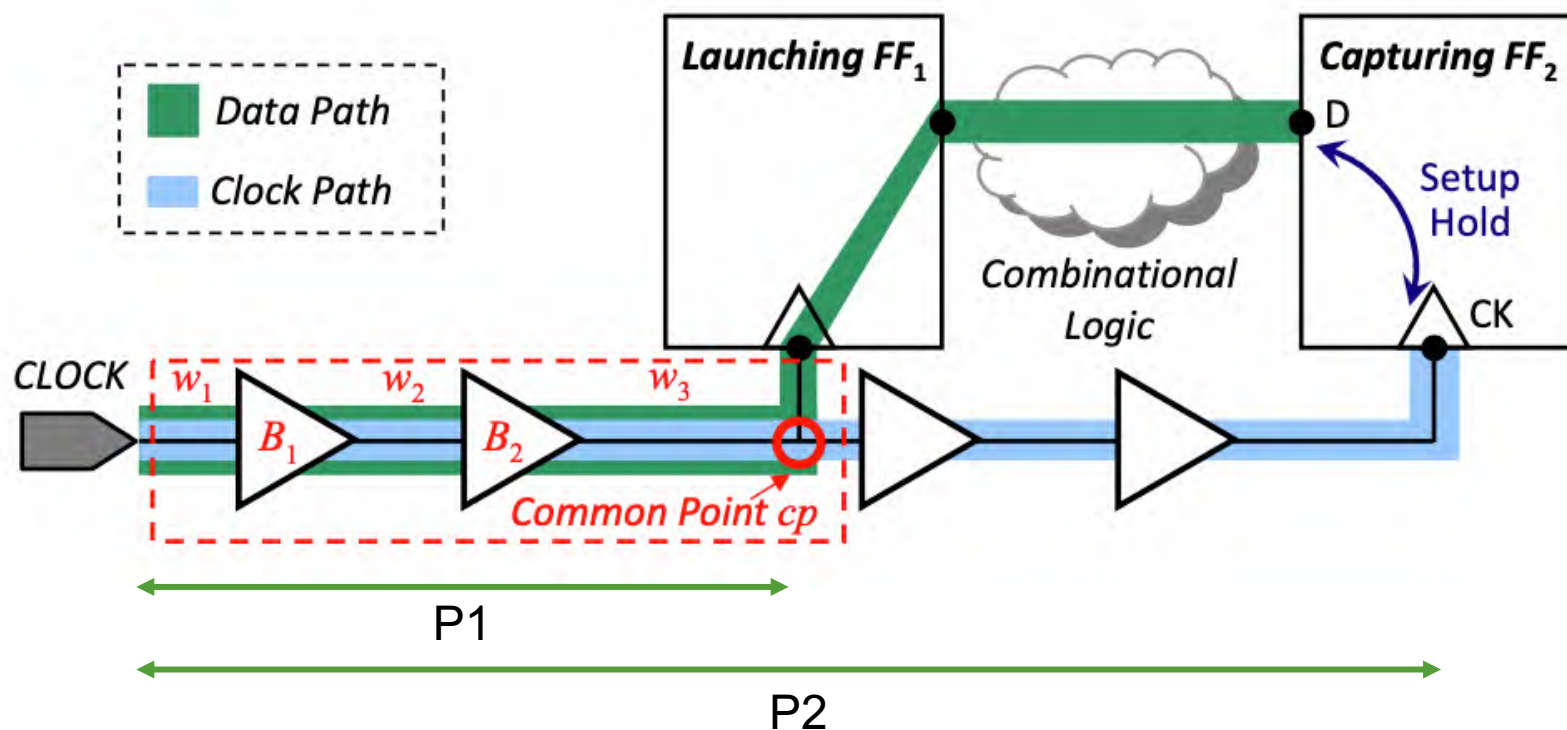
- **Hold tests:** $credit_{test}^{hold} = slack_{post-CPPR}^{hold} - slack_{pre-CPPR}^{hold}$
- **Setup tests:** $credit_{test}^{setup} = slack_{post-CPPR}^{setup} - slack_{pre-CPPR}^{setup}$



Common Path Pessimism Removal (CPPR)

Remove the pessimism on P1

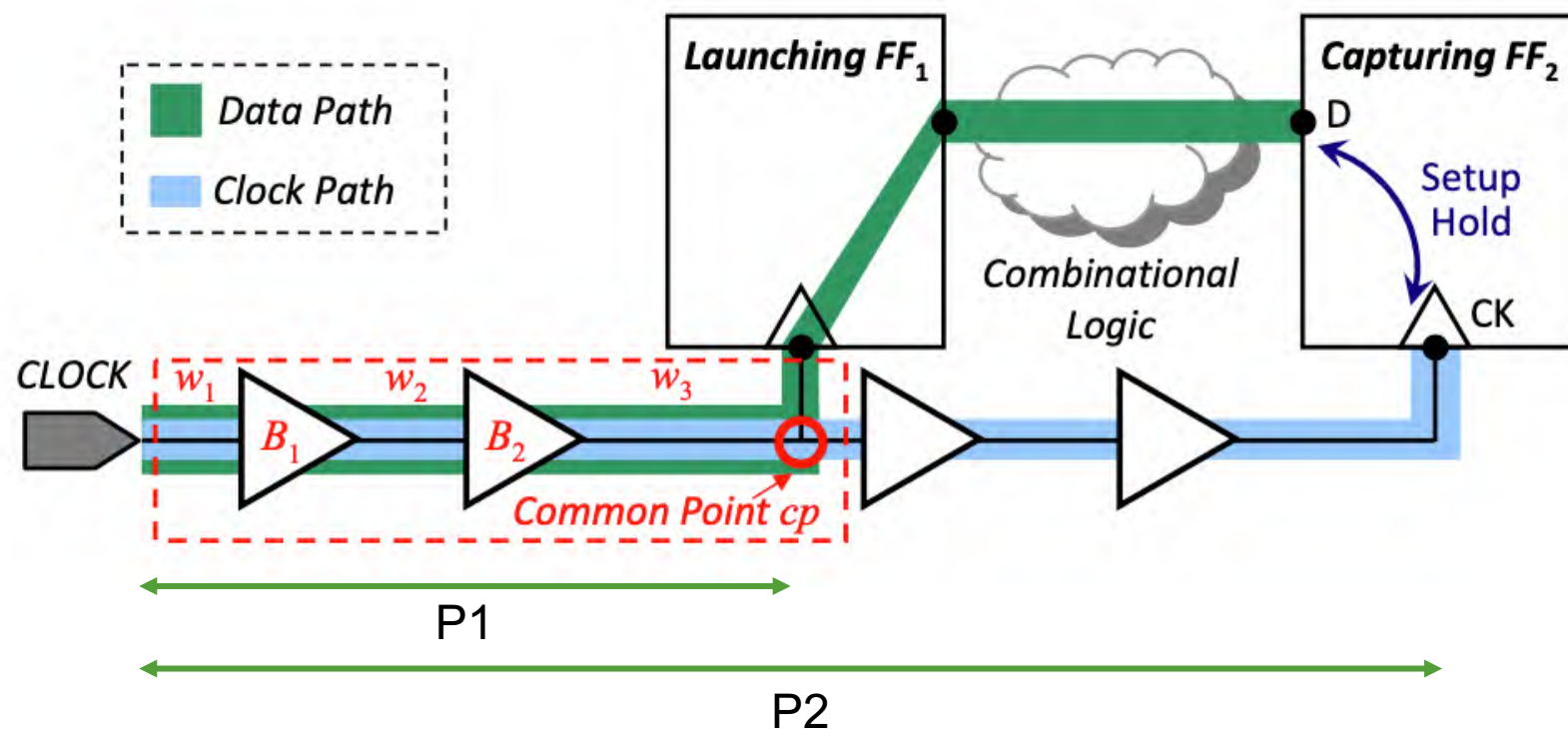- **Hold tests:** $credit^{hold} = AT_{cp}^{late} - AT_{cp}^{early}$
- **Setup tests:** $credit^{setup} = \sum_{p \in CP} (d_p^{late} - d_p^{early})$, $CP = \{w_1, B_1, w_2, B_2, w_3\}$



Common Path Pessimism Removal (CPPR)

Remove the pessimism on P1



– Hold tests: $credit^{hold} = AT_{cp}^{late} - AT_{cp}^{early}$

w. credit for clock root

w.o. credit for clock root

– Setup tests: $credit^{setup} = \sum_{p \in CP} (d_p^{late} - d_p^{early})$, $CP = \{w_1, B_1, w_2, B_2, w_3\}$

What's the difference?
Why different?

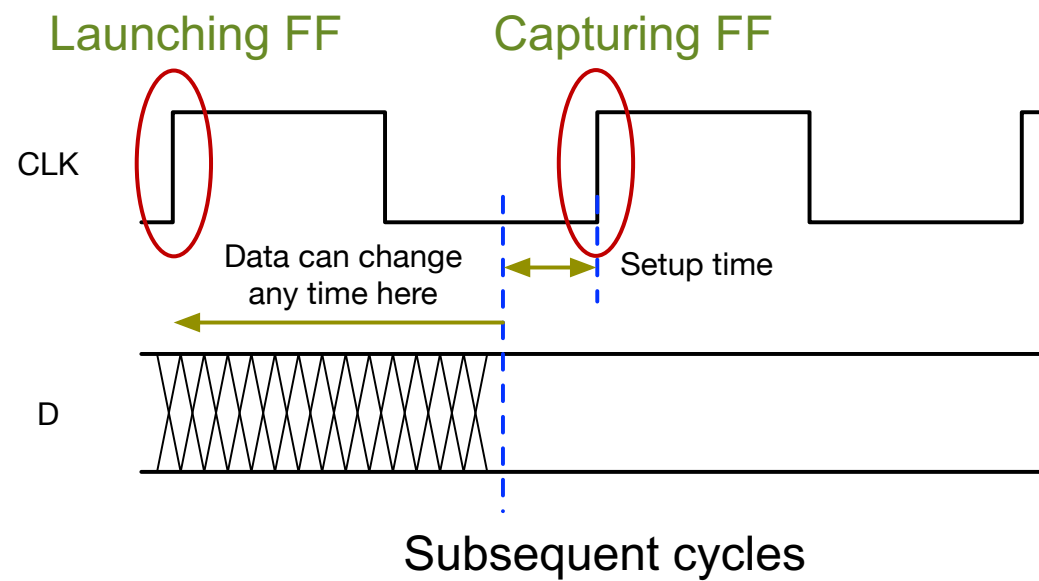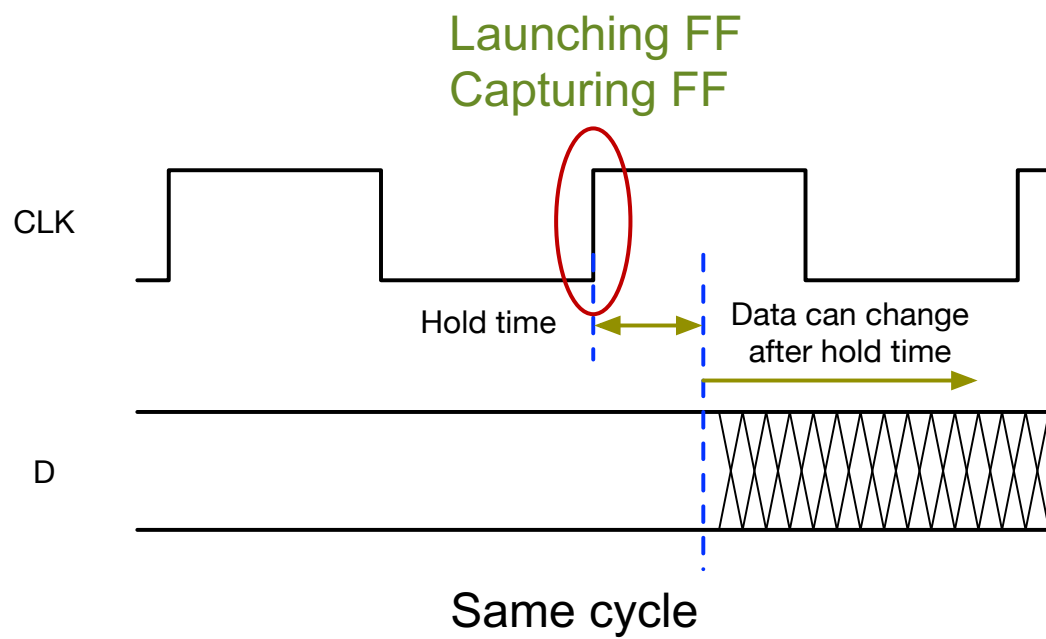

Early/late delay of clock root **CANCELLED OUT**

Exercise

Pre-CPPR Slack

$$\text{slack}_{FF3:D|DP1}^{\text{late}}$$

$$\text{slack}_{FF3:D|DP2}^{\text{late}}$$

Post-CPPR Slack


$$\text{credit}_{\text{setup}|DP1}$$

$$\text{credit}_{\text{setup}|DP2}$$

$$\text{slack}_{FF3:D|DP1}^{\text{late}, \text{Post-CPPR}}$$

$$\text{slack}_{FF3:D|DP2}^{\text{late}, \text{Post-CPPR}}$$

$$T_{CLK} = 120$$

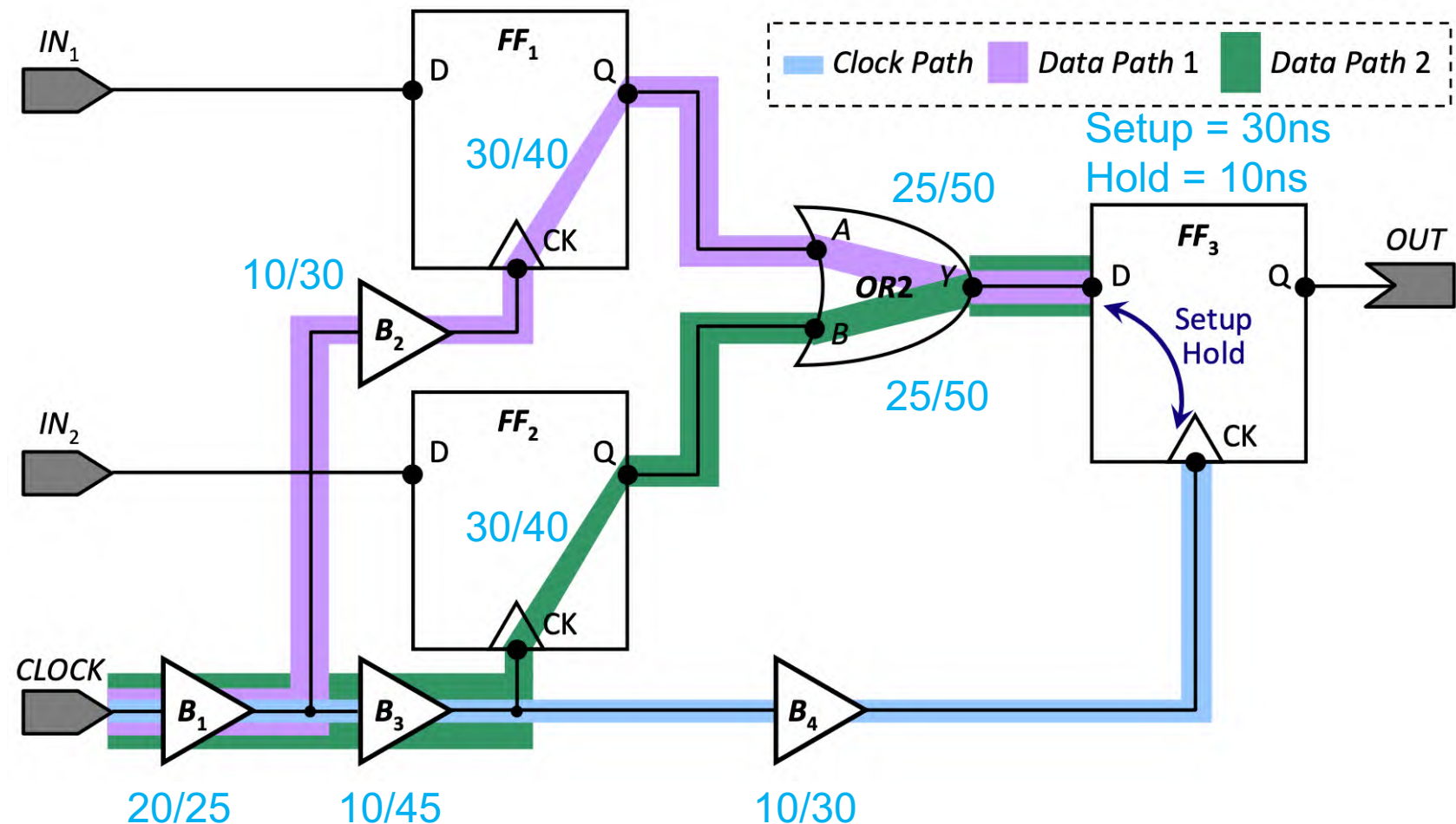

Exercise

$$slack_{FF3:D}^{late} = RAT_{FF3:D}^{late} - AT_{FF3:D}^{late} = T_{CLK} + AT_{FF3:CK}^{early} - t_{FF3}^{setup} - AT_{FF3:D}^{late}$$

$$\begin{aligned} slack_{FF3:D}^{late}|_{DP1} &= T_{CLK} + (d_{B1}^{early} + d_{B3}^{early} + d_{B4}^{early}) - t_{setup} - (d_{OR2:A \rightarrow OR2:Y}^{late} + d_{FF1:CK \rightarrow FF1:Q}^{late} + d_{B1}^{late} + d_{B2}^{late}) \\ &= 120 + (20 + 10 + 10) - 30 - (50 + 40 + 30 + 25) = -15 \end{aligned}$$


$$\begin{aligned} slack_{FF3:D}^{late}|_{DP2} &= T_{CLK} + (d_{B1}^{early} + d_{B3}^{early} + d_{B4}^{early}) - t_{setup} - (d_{OR2:B \rightarrow OR2:Y}^{late} + d_{FF2:CK \rightarrow FF2:Q}^{late} + d_{B1}^{late} + d_{B3}^{late}) \\ &= 120 + (20 + 10 + 10) - 30 - (50 + 40 + 45 + 25) = -30 \end{aligned}$$

$$credit_{setup}|_{DP1} = (d_{B1}^{late} - d_{B1}^{early}) = (25 - 20) = 5$$

$$\begin{aligned} credit_{setup}|_{DP2} &= (d_{B1}^{late} - d_{B1}^{early}) + (d_{B3}^{late} - d_{B3}^{early}) \\ &= (25 - 20) + (45 - 10) = 40 \end{aligned}$$


$$\begin{aligned} slack_{FF3:D}^{late}|_{DP1}^{Post-CPPR} &= slack_{FF3:D}^{late}|_{DP1} + credit_{setup}|_{DP1} \\ &= (-15 + 5) = -10 \end{aligned}$$

$$\begin{aligned} slack_{FF3:D}^{late}|_{DP2}^{Post-CPPR} &= slack_{FF3:D}^{late}|_{DP2} + credit_{setup}|_{DP2} \\ &= (-30 + 40) = 10 \end{aligned}$$

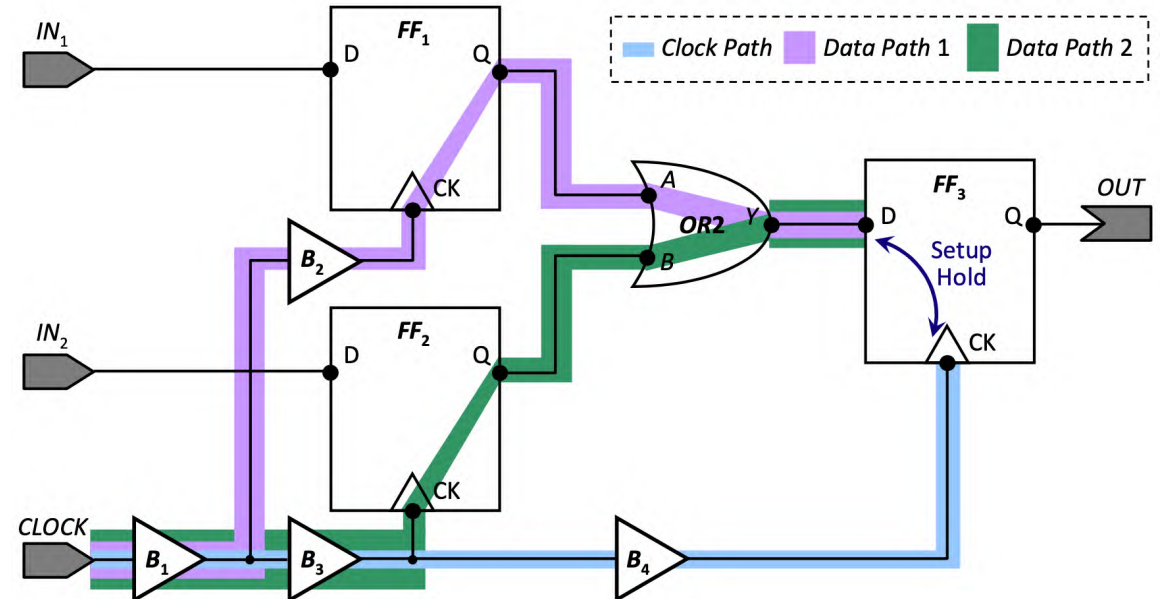

Basic Idea in CPPR Algorithms


- Enumerate paths
 - Pairs of launching and capturing FFs
- Compute lowest common ancestor (LCA) for each pair
- Naïve method
 - Find a path from root to FF1:Clk and store it in a vector
 - Find a path from root to FF2:Clk and store it in a vector
 - Traverse both paths till the values in the vectors are the same
 - Time complexity $O(n)$, where n is #nodes in the clock tree
 - Better algorithms exist
- Generate top-k paths

 


Improved CPPR Algorithms

- Tsung-Wei Huang, P.-C. Wu, and Martin Wong, “[UI-Timer: An ultra-fast clock network pessimism removal algorithm](#)”, in Proc. ICCAD, pp. 596-599, 2014.
- P.-Y. Lee, I. H.-R. Jiang, C.-R. Li, W.-L. Chiu, and Y.-M. Yang, “[iTimerC 2.0: Fast incremental timing and cppr analysis](#),” in Proc. ICCAD. IEEE, 2015, pp. 890–894.
- B. Jin, G. Luo, and W. Zhang, “[A fast and accurate approach for common path pessimism removal in static timing analysis](#),” in Proc. ISCAS. IEEE, 2016, pp. 2623–2626.
- C. Peddawad, A. Goel, B. Dheeraj, and N. Chandrachoodan, “[iitrace: A memory efficient engine for fast incremental timing analysis and clock pessimism removal](#),” in Proc. ICCAD, 2015, pp. 903–909.
- T. Chung-Hao and M. Wai-Kei, “[A fast parallel approach for common path pessimism removal](#),” in Proc. ASPDAC, 2015, pp. 372–377.
- Z. Guo, M. Yang, T. Huang, and Y. Lin, “[A Provably Good and Practically Efficient Algorithm for Common Path Pessimism Removal in Large Designs](#)”, in IEEE TCAD, 2021

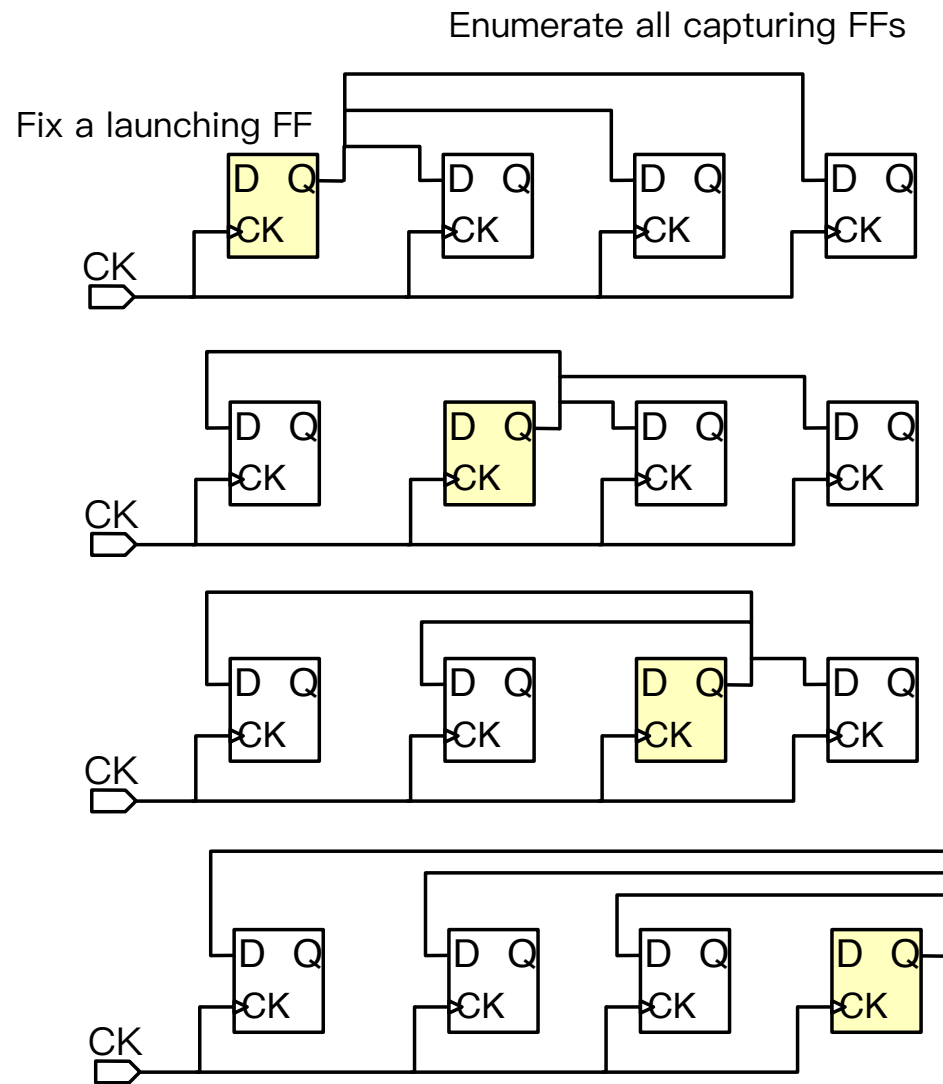CPPR with FF enumeration [Huang, ICCAD'14]




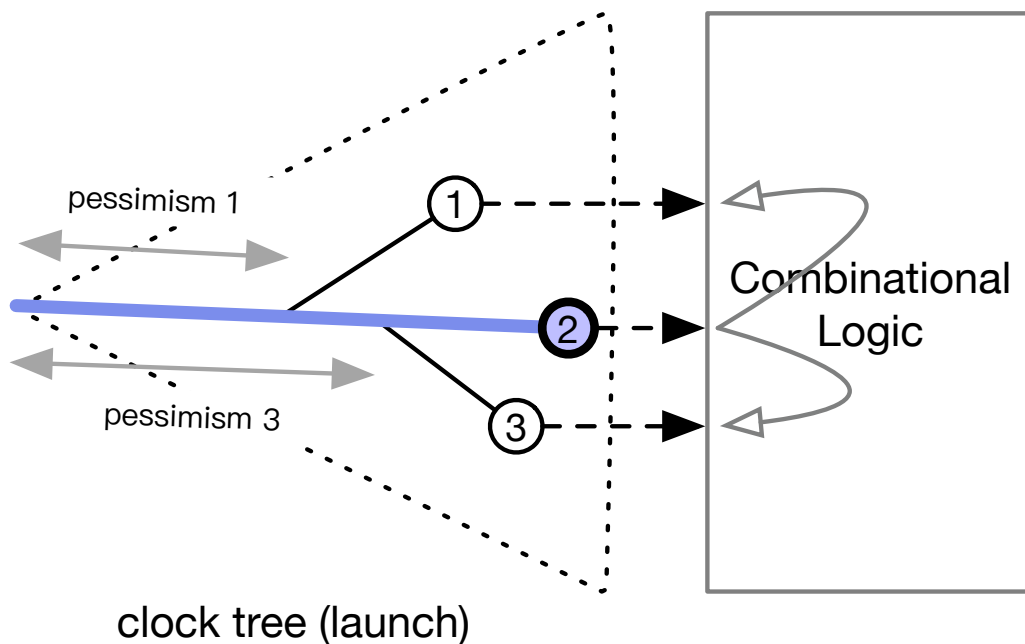- Fix a launching FF and enumerate all capturing FFs (or, fix a capturing FF and enum. all launching FFs)
- Construct a Pessimism-Free Graph
 - Offset the arrival time by the CPPR credits in advance







CPPR with FF enumeration [Huang, ICCAD'14]

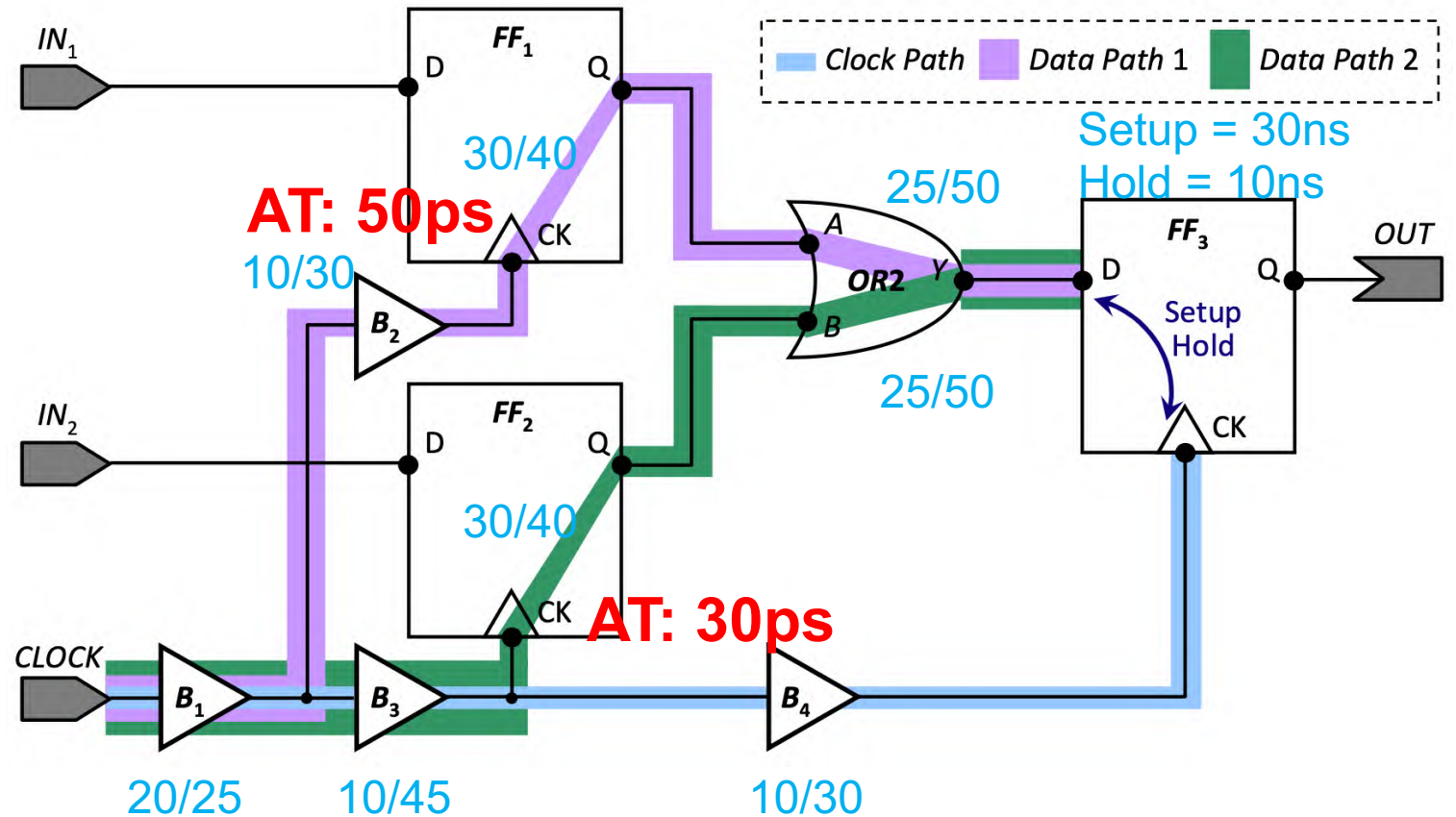- Example
- Fix FF3 as capturing FF
- Compute credits:
 - FF1, FF3: 5ps
 - FF2, FF3: 40ps
- Add credits to arrival time
 - FF1.CK: $25 + 30 - 5 = 50\text{ps}$
 - FF2.CK: $25 + 45 - 40 = 30\text{ps}$
- Propagate the arrival time
=> Pessimism-Free Graph
- Compute all paths that arrive at FF3, ignoring other destinations; Repeat the process for other capturing FFs.




CPPR with Depth Enumeration [Guo, DAC'21]

- #FFs > 10,000. FF enumeration is very slow, but clock tree depth $D < 100$.
- Solution: identify FF pairs with **lowest common ancestors (LCA) of depth $d=0,1,\dots,D-1$** , and process these FF pairs in a single propagation.
- The clock edges above the fixed depth d are recognized as common paths.
- Computation repeated for different d , instead of different launching FFs/capturing FFs. => 1000x fewer iters!

    

CPPR with Depth Enumeration [Guo, DAC'21]

 
- A depth d fixed. How to find all FF pairs with such LCA depth?
- Solution: Group the FFs by their depth- $d+1$ ancestors.
- If launching FF and capturing FF come from the same group, they have unhandled pessimism (red tree edge below)



Group Constraint:
Launching FF and capturing FF must come from different groups.

CPPR with Depth Enumeration [Guo, DAC'21]

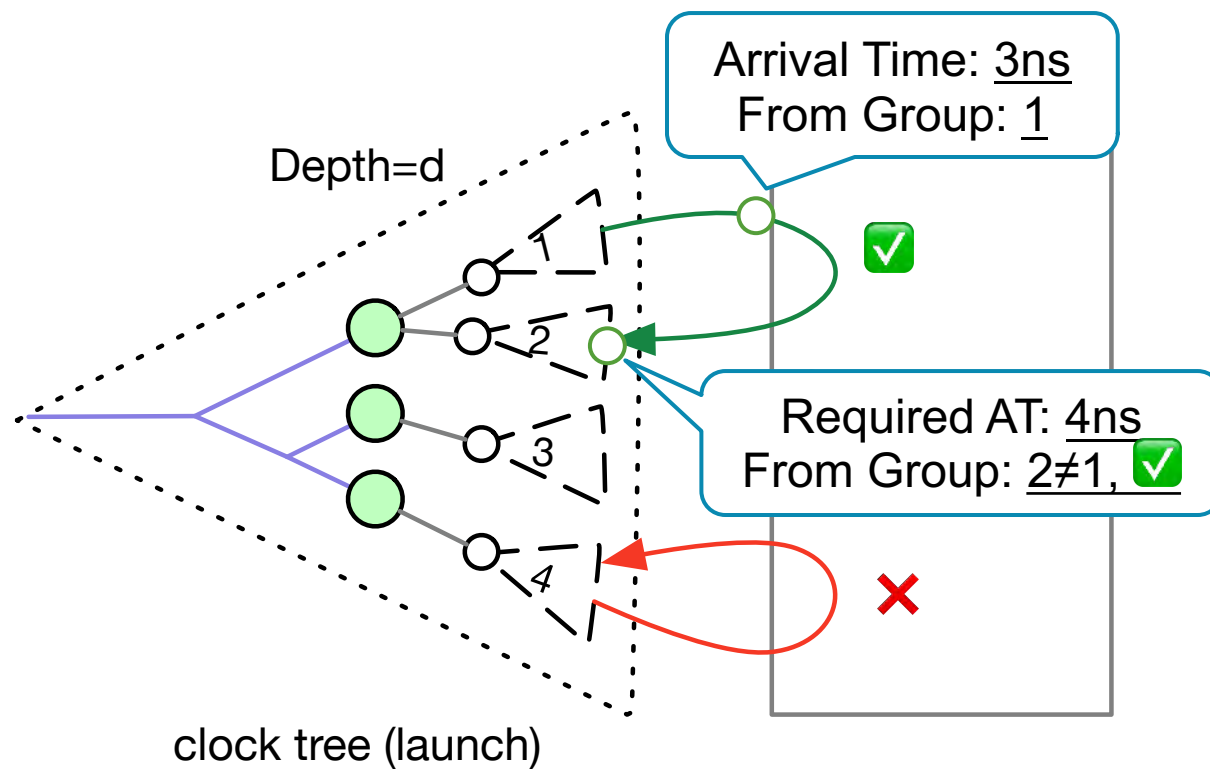- How to enforce the group constraint when we propagate the arrival times?
- Solution: propagate the arrival time with a **tag** on its launching FF's group index.



CPPR with Depth Enumeration [Guo, DAC'21]

Example


Fix depth $d=1$

- Only B1 on common path.
- Arrival Times:
FF1.CK: 50ps, FF2.CK: 65ps,
FF3.CK:

Groups

- Group 1: {FF1}
- Group 2: {FF2, FF3}

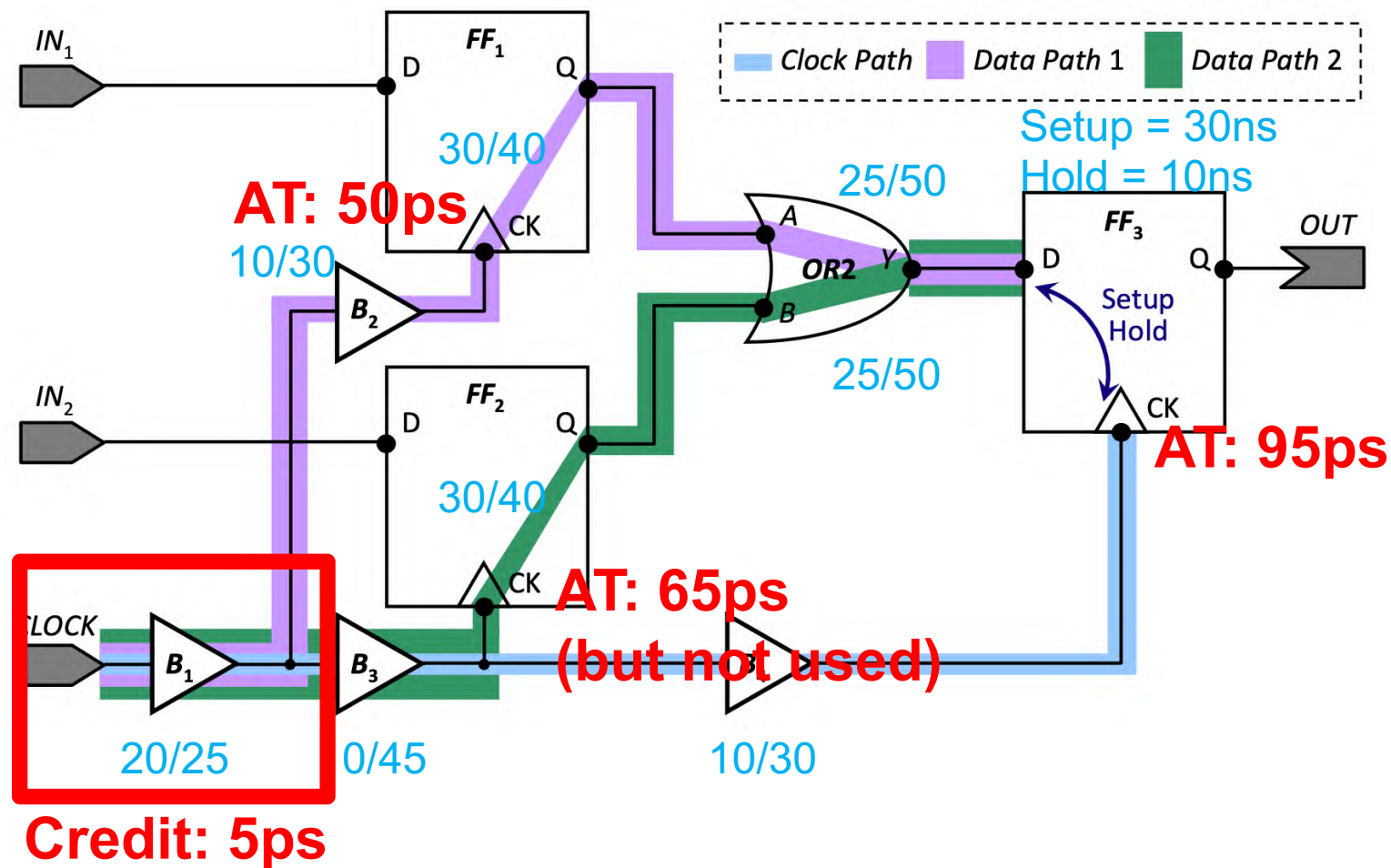
- Data path 1 valid,
path 2 invalid (same group)



Generate Top-1 Critical Path


► Working on DAG

 - Setup check: longest path
- Hold check: shortest path



Generate Top-K Critical Paths

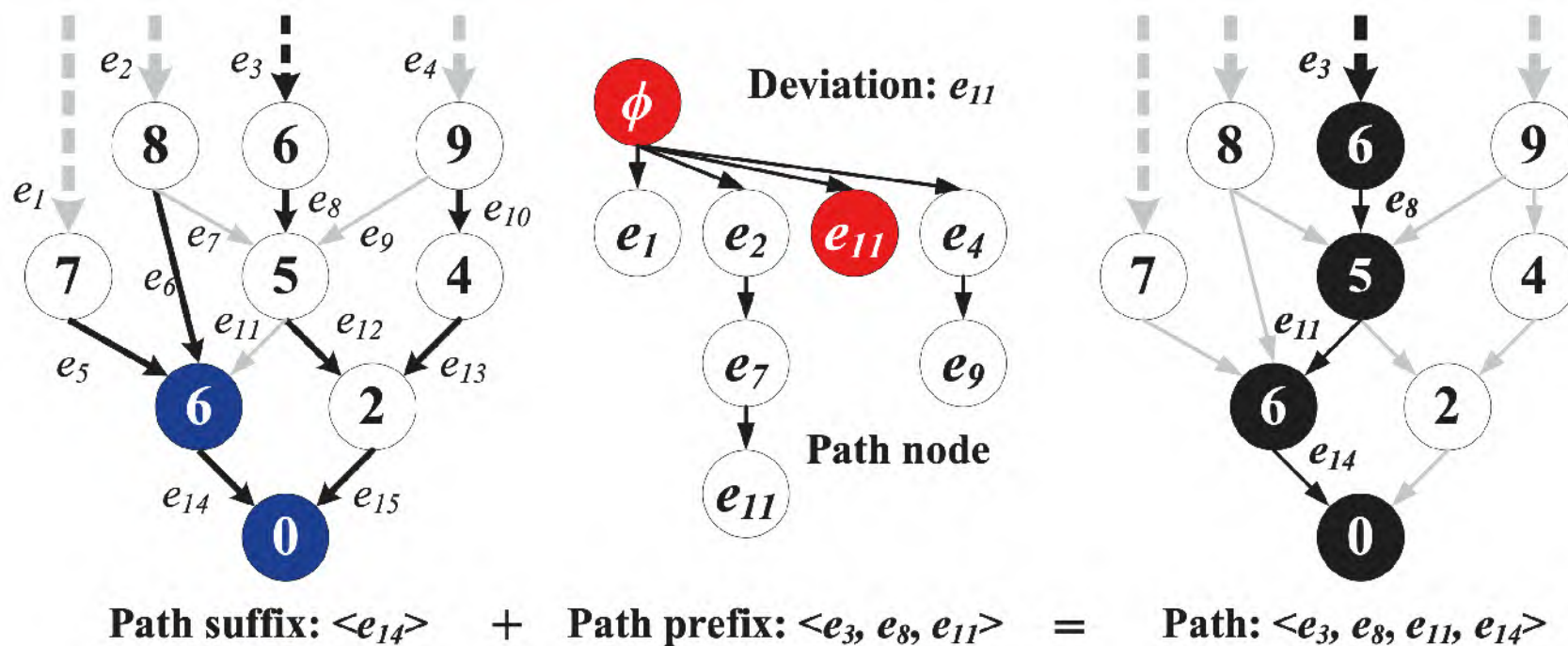- OpenTimer adopts implicit path representation
 - Each path is represented using $O(1)$ space and time
 - Each path is ranked through a *prefix* tree & a *suffix* tree



Summary

- Net delay
 - Elmore delay
- Cell delay
 - Lookup table
- Graph-based analysis
 - Setup time, hold time
 - Arrival time, required arrival time, slack
- Path-based analysis
 - CPPR

Other Topics

- Incremental timing analysis (TAU [2015](#) contest)
- Timing macros (TAU [2016-2017](#) contest)
- Timing reports (TAU [2018](#) contest)
- Timing-driven design optimization (TAU [2019](#) contest)
- Current source delay models (TAU [2020](#) contest)